

# **MIPS32: Single-Cycle CPU**

**Seungwan Noh**

*Pusan National University*

*Department of Electronics Engineering*

# Contents


---

- Instruction Set Architecture
- Single-cycle CPU Design
- Verilog HDL Implementation
- Simulation
- References
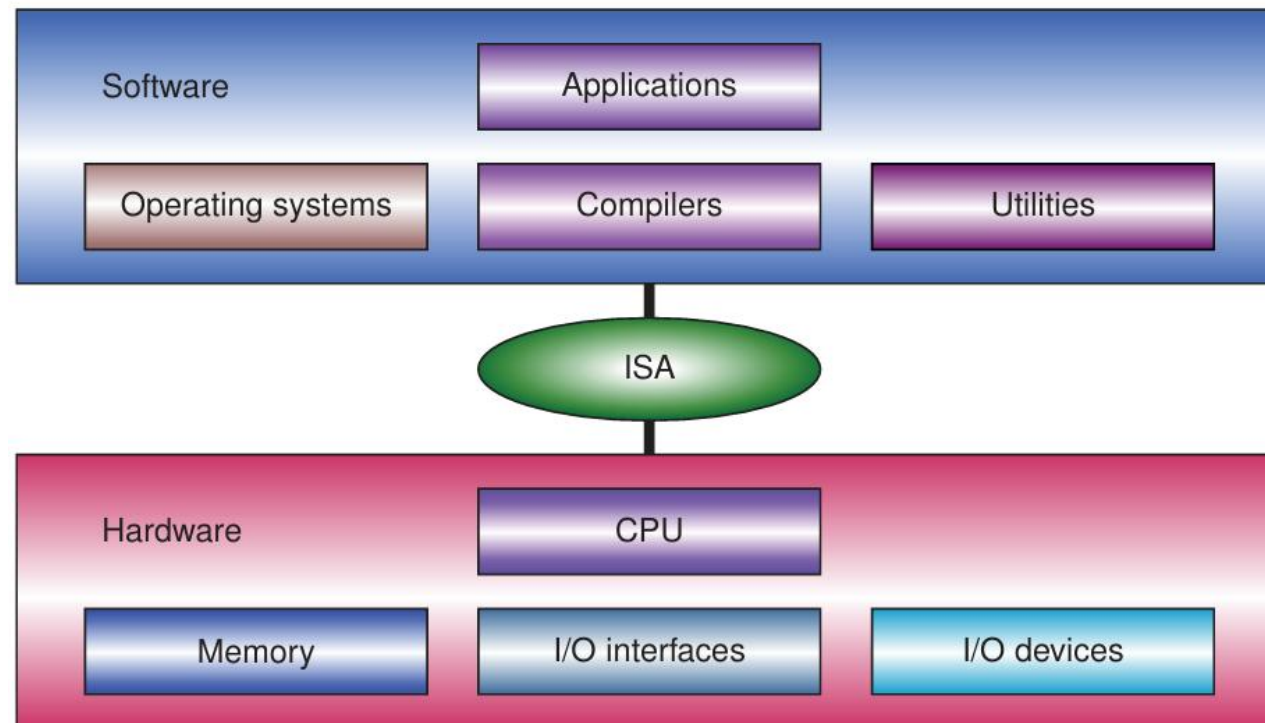
# Instruction Set Architecture

---

- “What a CPU should do.”
- CPU designers design a CPU to implement the ISA.
- An interface between SW and HW.



# Instruction Set Architecture

- Operand types

Operand type	Bits	Value range	Corresponding to C
Byte	8	−128 to +127	signed char
Unsigned byte	8	0 to 255	unsigned char
Half word	16	−32,768 to +32,767	short int
Unsigned half word	16	0 to 65,535	unsigned short int
Word	32	−2,147,483,648 to +2,147,483,647	int
Unsigned word	32	0 to 4,294,967,295	unsigned int
Single-precision FP	32		float
Double-precision FP	64		double

# Instruction Set Architecture


---

- Instruction types
  - ✓ Arithmetic operation
  - ✓ Logic operation
  - ✓ Shift operation
  - ✓ Memory access
  - ✓ I/O access
  - ✓ Control transfer
  - ✓ Floating-point calculation
  - ✓ System control
 
# Instruction Set Architecture

---

- Register-register architecture
  - ✓ All operands are explicitly in a general-purpose register file.
  - ✓ Almost all RISC type ISAs use this architecture.



# Instruction Set Architecture

---

## ■ Addressing Modes

### ✓ Register Operand Addressing

- The operand is in a register file.
- *add r3, r1, r2*

### ✓ Immediate Addressing

- The operand is in instruction.
- *addi r1, r1, -1*

### ✓ Direct Addressing

- The operand is in the memory whose address is given in the instruction.
- *add r3, r1, [0x1234]*

### ✓ Register Indirect Addressing

- The operand is in the memory whose address is given by a register.
- *add r3, r1, (r2)*

### ✓ Offset Addressing

- The operand is in the memory whose address is the sum of an offset and a register.
- *add r3, r1, 0x1234(r2)*


# Instruction Set Architecture

---

- MIPS32 Instruction Format and Registers
- R (register)
  - ✓ *op* is 0, the operation is specified by *func*.
  - ✓ *Shift* instruction use *sa* to specify the shift amount, *rt* is shifted to *rd*.
  - ✓ Other R-format read *rs*, *rt* and write the result to *rd*.
- I (immediate)
  - ✓ Use *immediate* as the second source operand.
  - ✓ The 16-bit *immediate* must be sign-extended into 32 bits.
  - ✓ The first source operand is *rs*, and the result is written into *rt*.
  - ✓ The conditional branch compare *rs* and *rt*, *immediate* as an offset for the branch target address.
  - ✓ The load/store instructions load/store data of *rt* to memory, the memory address is the sum of *rs* and *immediate*.
- J (jump)
  - ✓ Shifted to the left by 2 bits to form a low 28 bits of the jump target address.



# Instruction Set Architecture

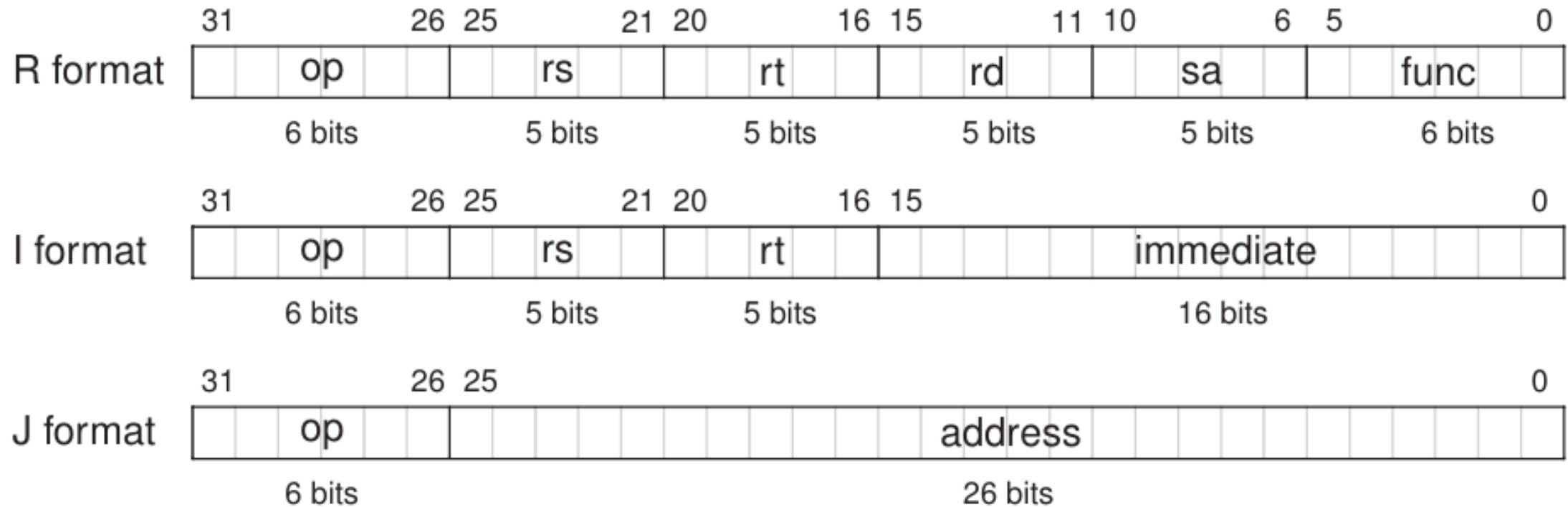

# Instruction Set Architecture

- MIPS general-purpose registers

Register name	Register number	Use
\$zero	0	Constant 0
\$at	1	Assembler temporary
\$v0 to \$v1	2 to 3	Function return value
\$a0 to \$a3	4 to 7	Function parameters
\$t0 to \$t7	8 to 15	Temporaries
\$s0 to \$s7	16 to 23	Saved temporaries
\$t8 to \$t9	24 to 25	Temporaries
\$k0 to \$k1	26 to 27	Reserved for OS kernel
\$gp	28	Global pointer
\$sp	29	Stack pointer
\$fp	30	Frame pointer
\$ra	31	Return address

# Instruction Set Architecture

## ■ 20 MIPS integer instructions


Inst.	[31:26]	[25:21]	[20:16]	[15:11]	[10:6]	[5:0]	Meaning
add	000000	rs	rt	rd	00000	100000	Register add
sub	000000	rs	rt	rd	00000	100010	Register subtract
and	000000	rs	rt	rd	00000	100100	Register AND
or	000000	rs	rt	rd	00000	100101	Register OR
xor	000000	rs	rt	rd	00000	100110	Register XOR
sll	000000	00000	rt	rd	sa	000000	Shift left
srl	000000	00000	rt	rd	sa	000010	Logical shift right
sra	000000	00000	rt	rd	sa	000011	Arithmetic shift right
jr	000000	rs	00000	00000	00000	001000	Register jump
addi	001000	rs	rt		Immediate		Immediate add
andi	001100	rs	rt		Immediate		Immediate AND
ori	001101	rs	rt		Immediate		Immediate OR
xori	001110	rs	rt		Immediate		Immediate XOR
lw	100011	rs	rt		offset		Load memory word
sw	101011	rs	rt		offset		Store memory word
beq	000100	rs	rt		offset		Branch on equal
bne	000101	rs	rt		offset		Branch on not equal
lui	001111	00000	rt		immediate		Load upper immediate
j	000010			address			Jump
jal	000011			address			Call

# Single-Cycle CPU Design

---


- A single-cycle CPU executes each instruction in one clock cycle.
- The most cost-effective but time-consuming CPU.
- The circuits for instruction fetch
  - ✓ PC points to a memory location of instructions.
  - ✓ The instruction in the location will be executed by the CPU.
  - ✓ PC is a byte address.
  - ✓ Incremented by 4 because instruction is 32 bits (4 bytes).
- The circuits for instruction execution
  - ✓ ALU
  - ✓ Register File
  - ✓ Control Unit

# Single-Cycle CPU

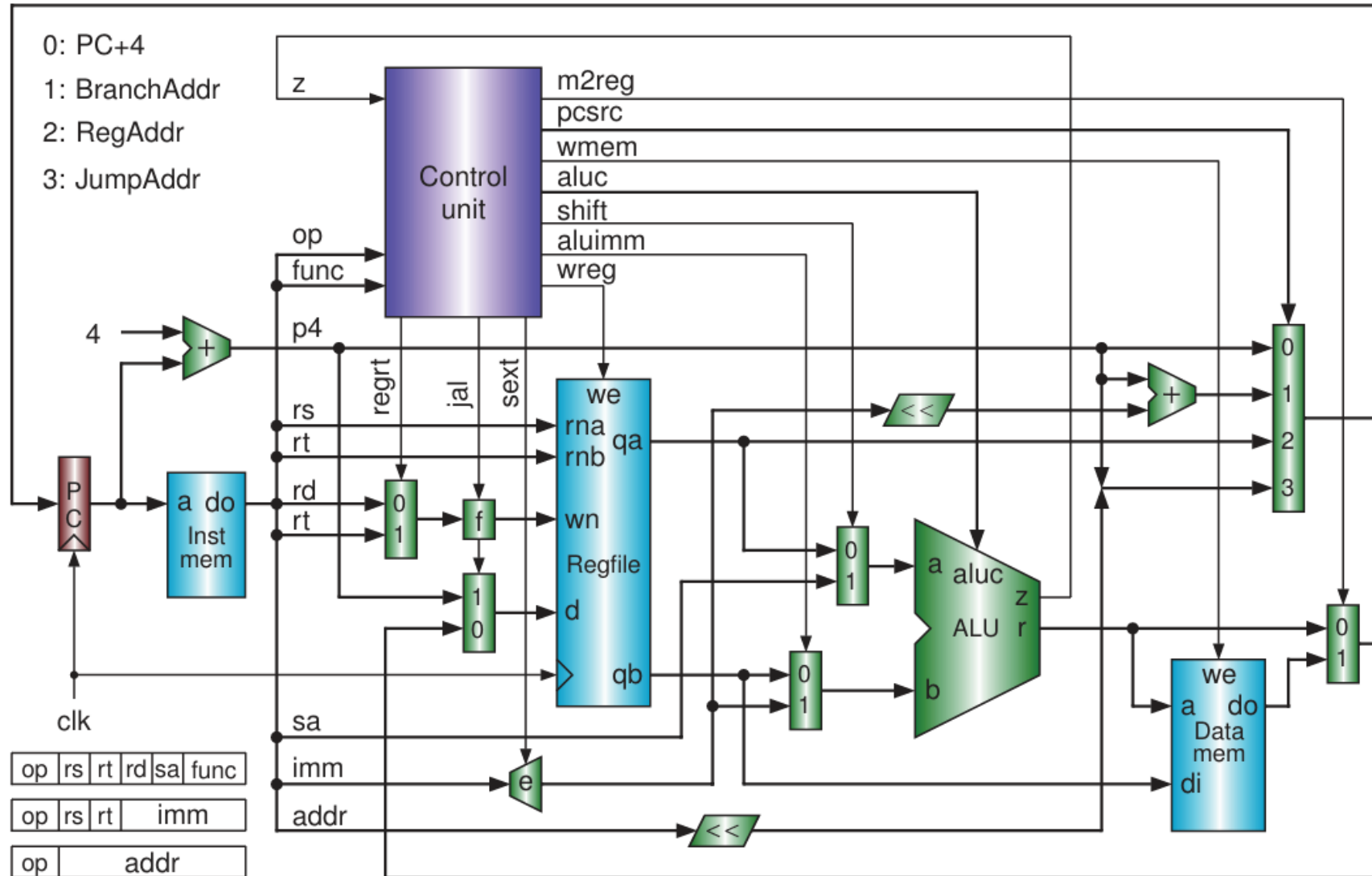

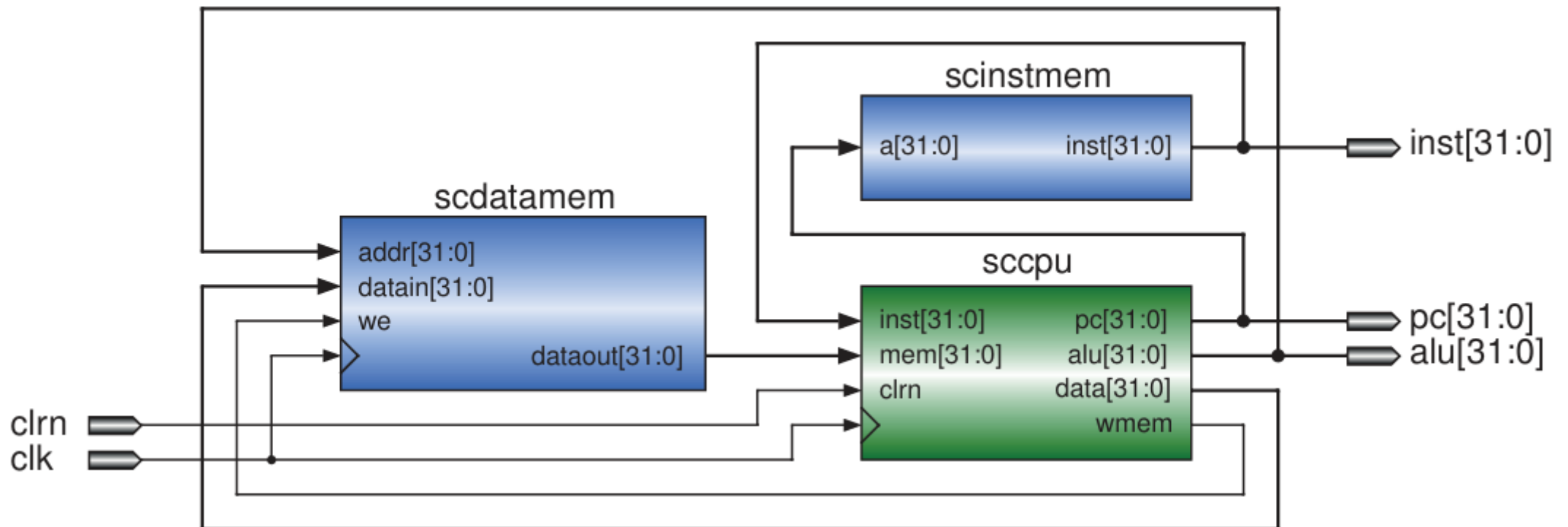
# Single-Cycle CPU

- Implement an instruction cache and a data cache inside the CPU so that only one off-chip memory module can be used for storing both the program and data.



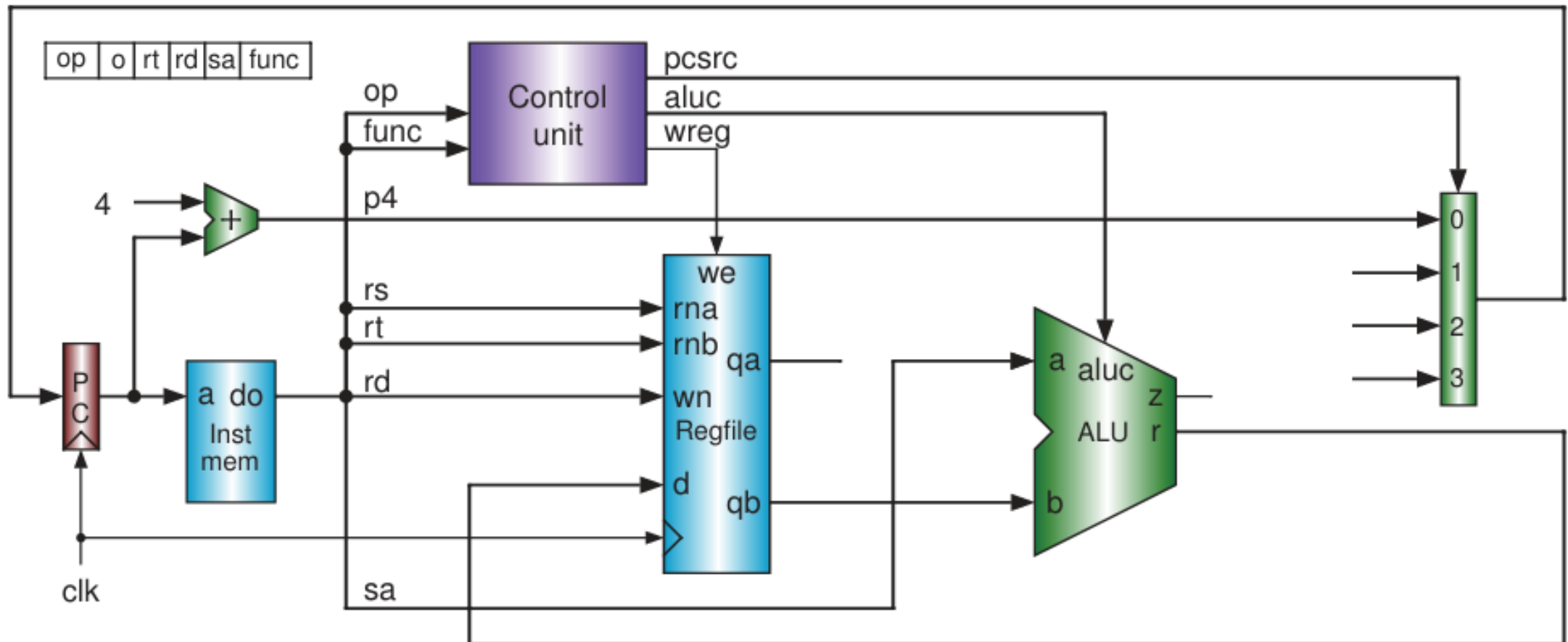
# Single-Cycle CPU Design

- The circuits required by R-format instructions.


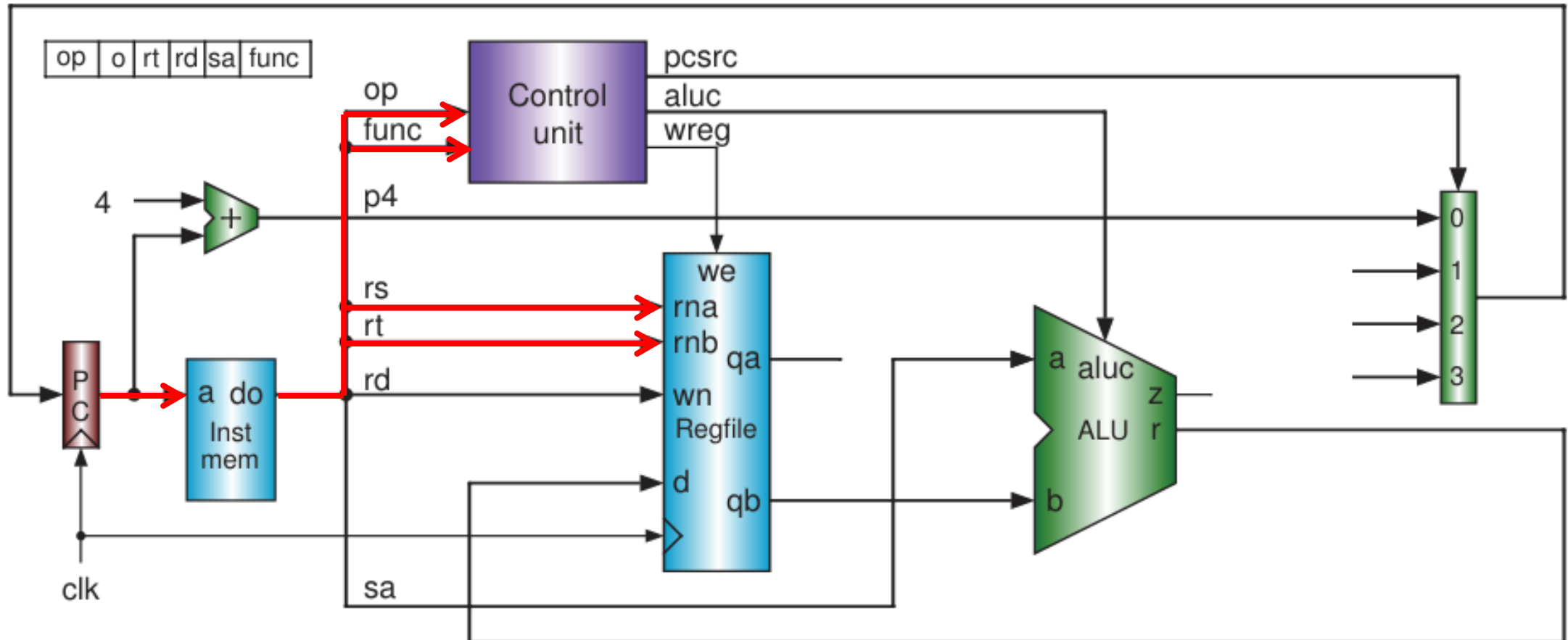
# Single-Cycle CPU Design


- *add/sub/and/or/xor* (instruction fetch)






# Single-Cycle CPU Design

- *sll/srl/sra* (instruction fetch)

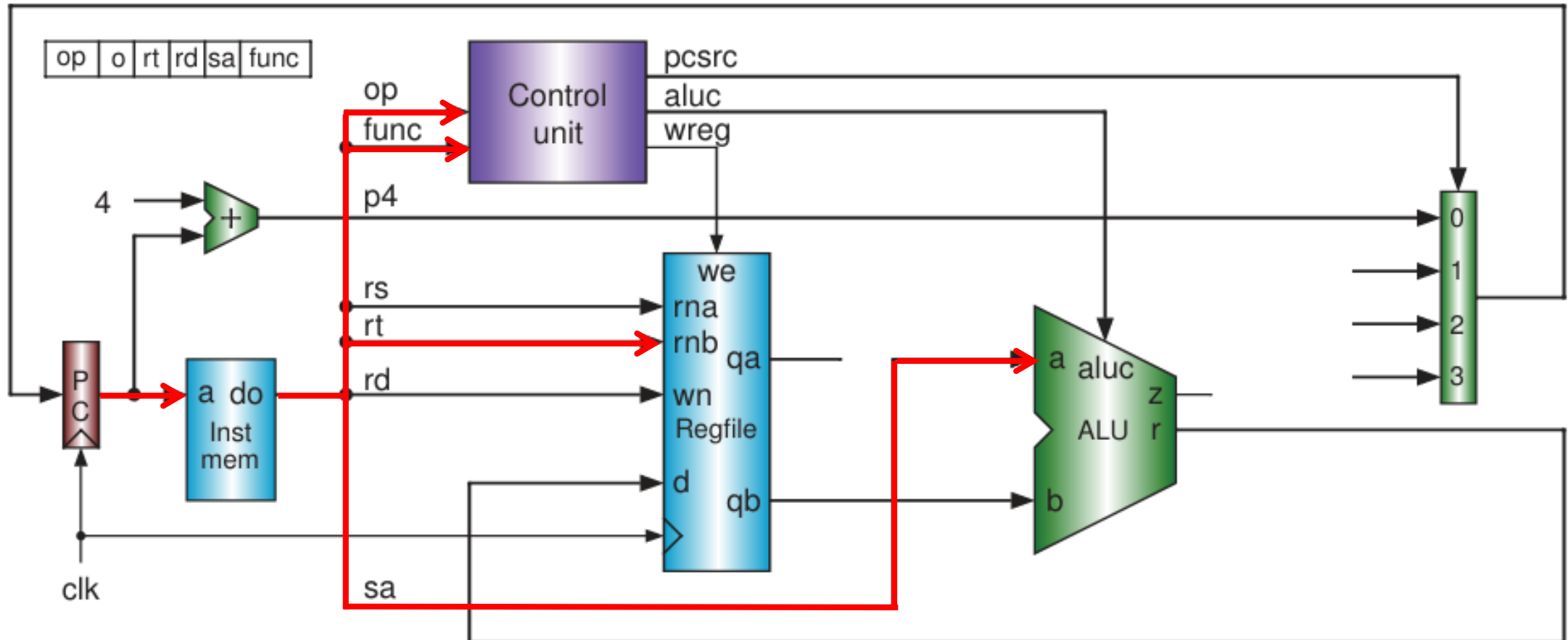

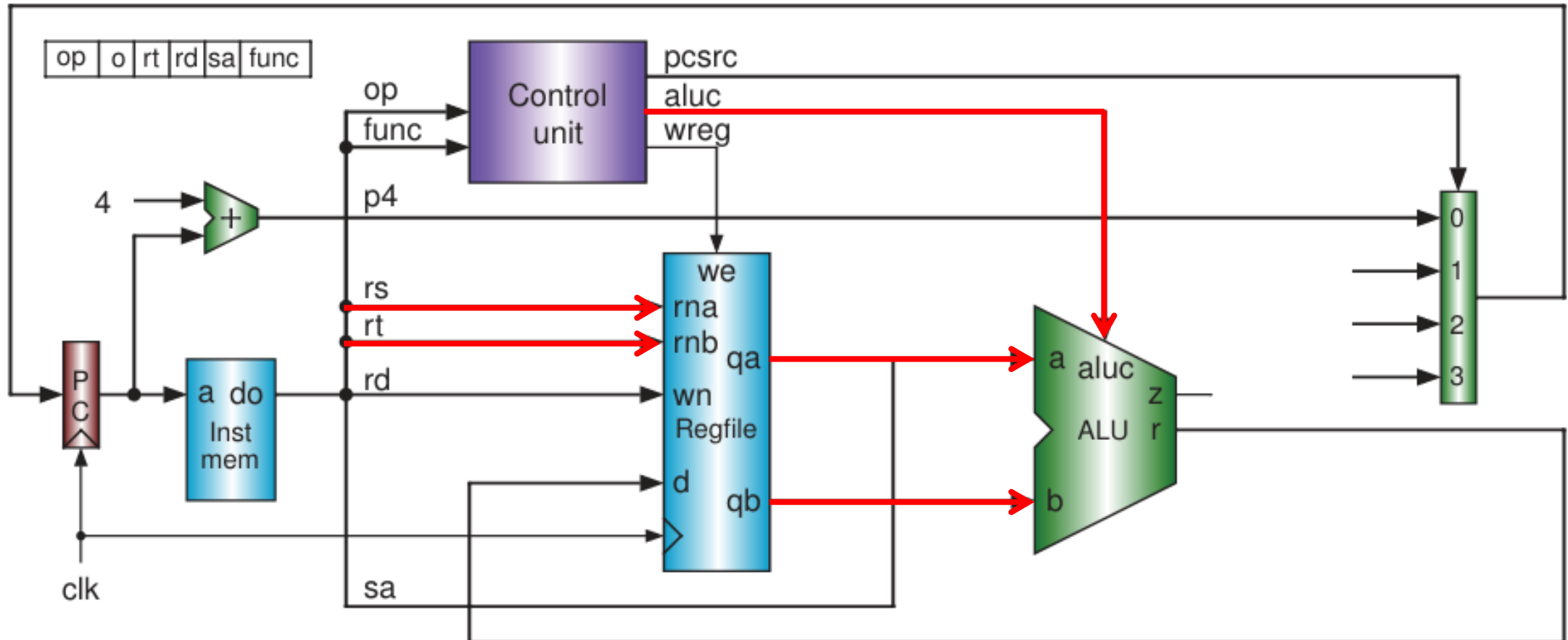
# Single-Cycle CPU Design

- *add/sub/and/or/xor* (instruction execute)




# Single-Cycle CPU Design

- *add/sub/and/or/xor* (write back)

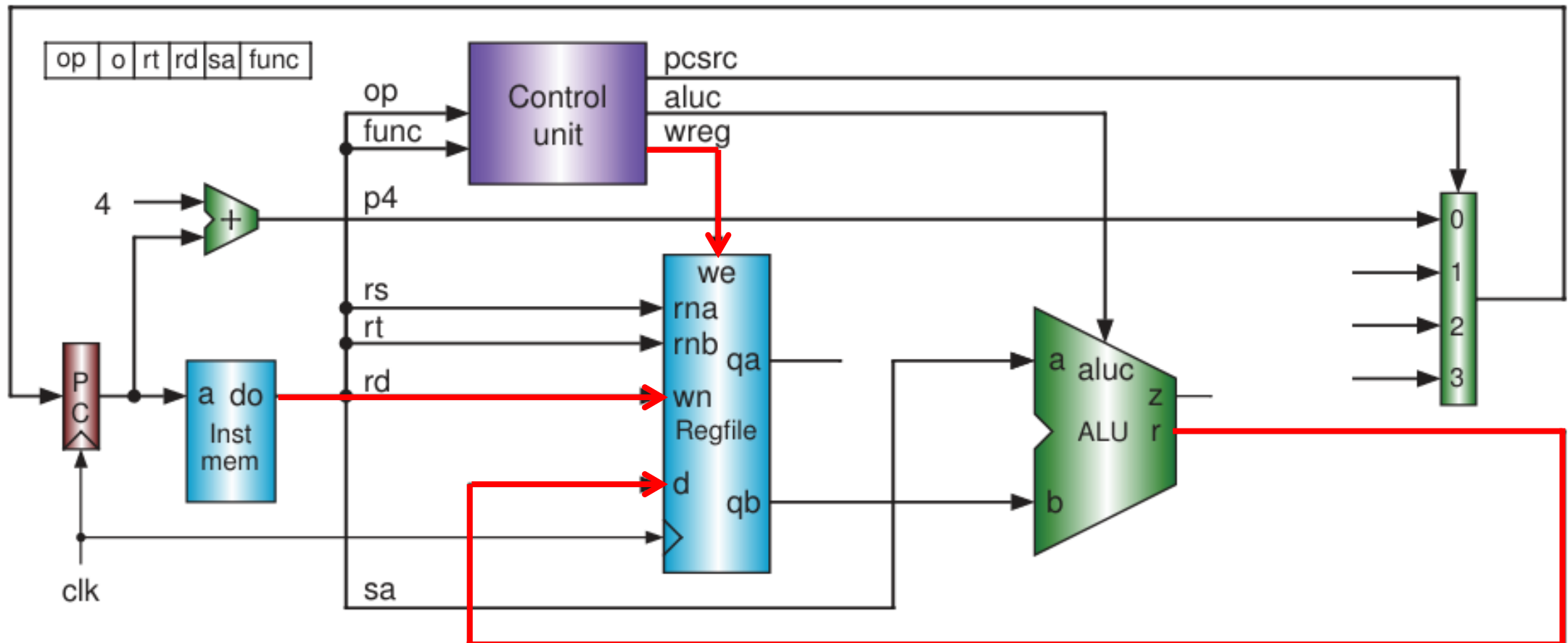
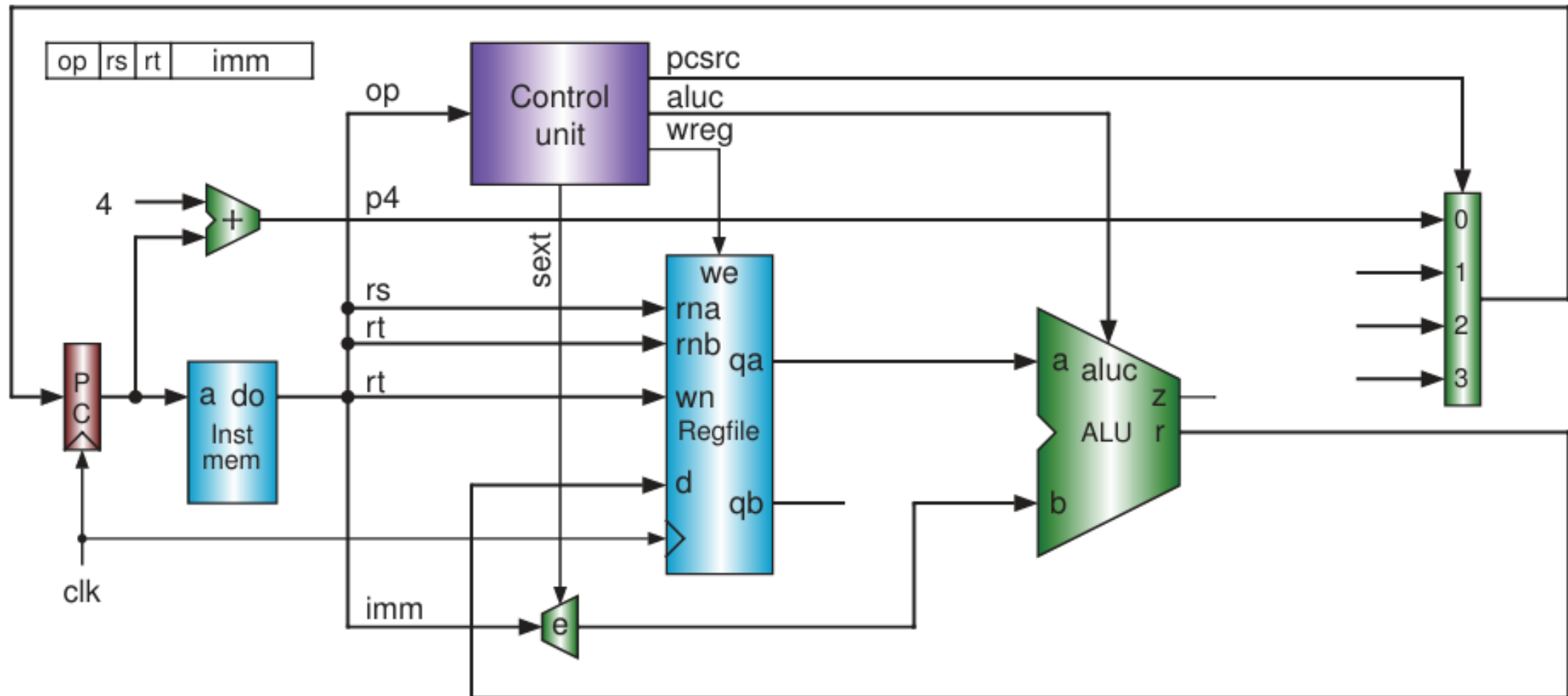
# Single-Cycle CPU Design


- The circuits required by I-format instructions.





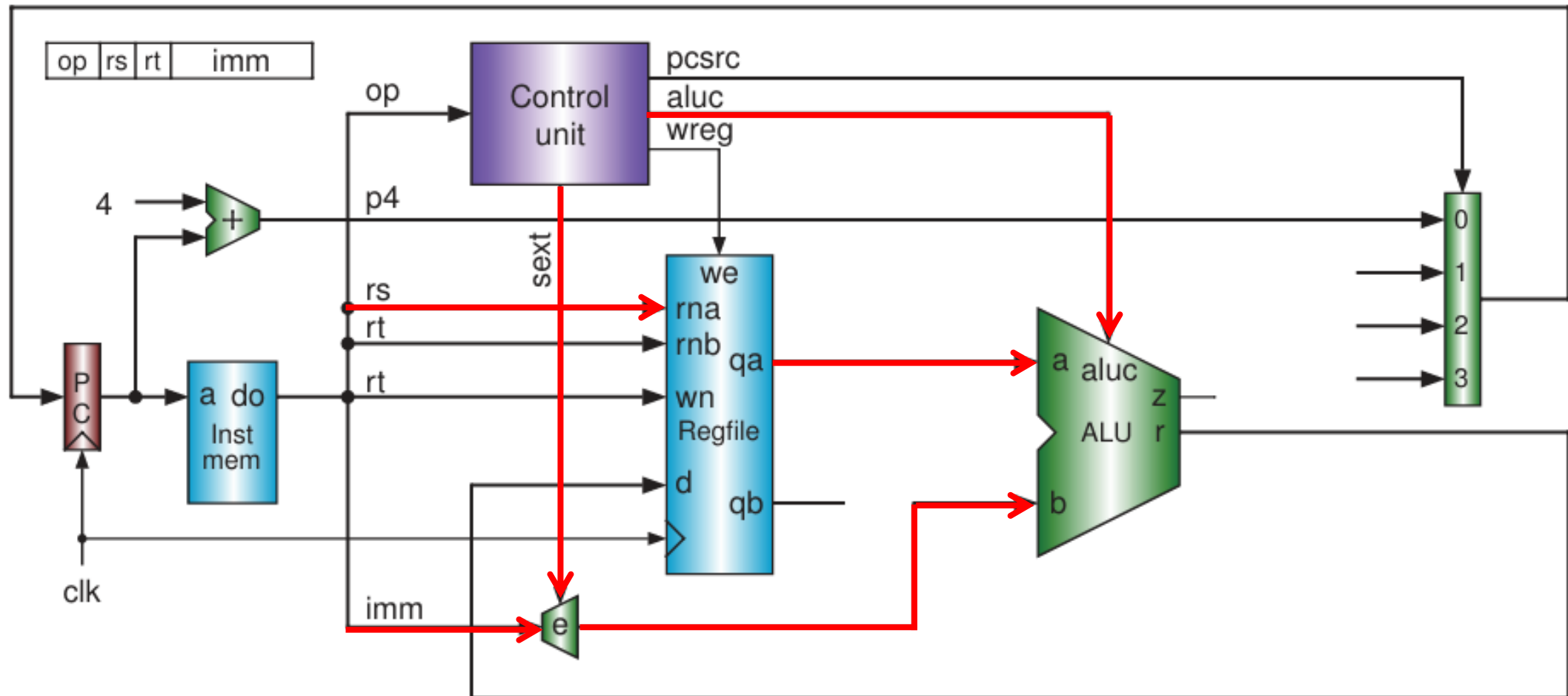
# Single-Cycle CPU Design

- *addi/andi/ori/xori/lui* (instruction execute)




# Single-Cycle CPU Design

- *addi/andi/ori/xori/lui* (write back)

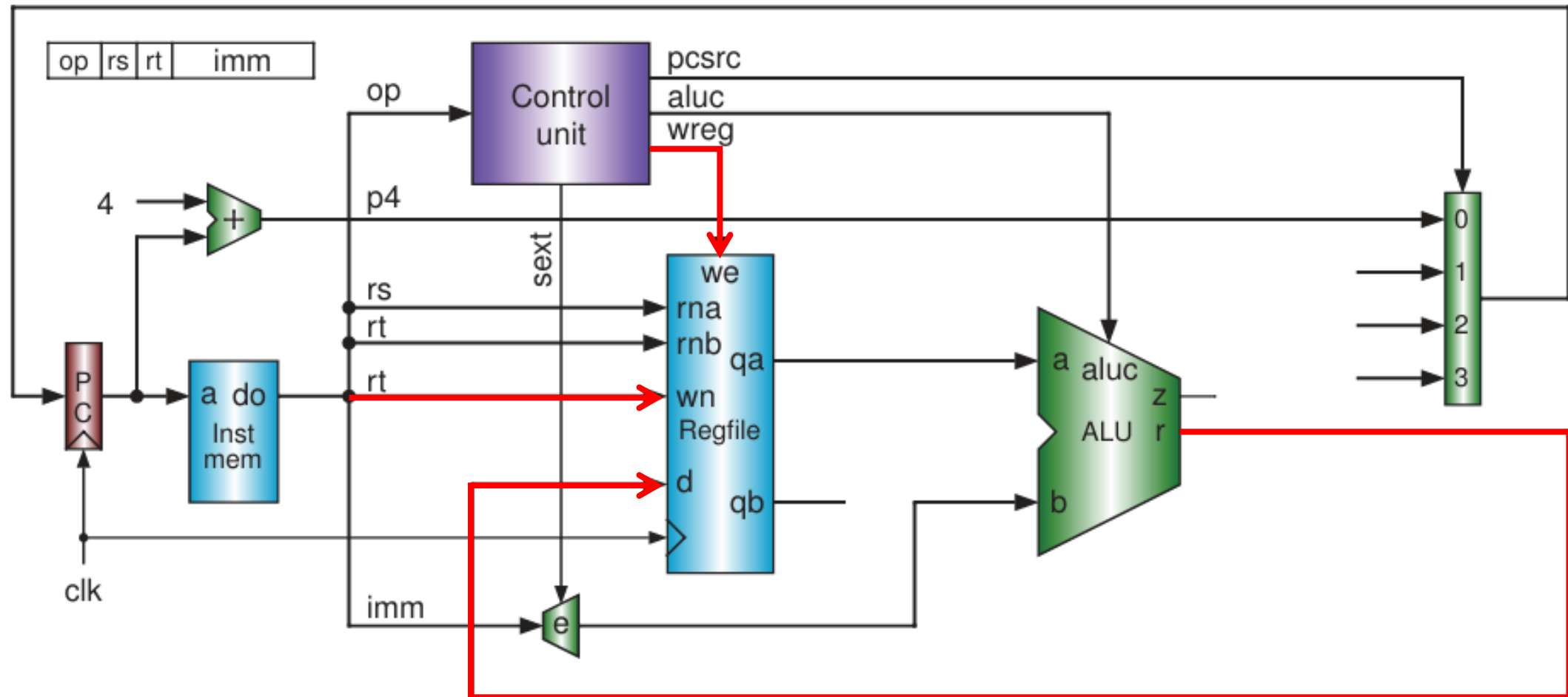
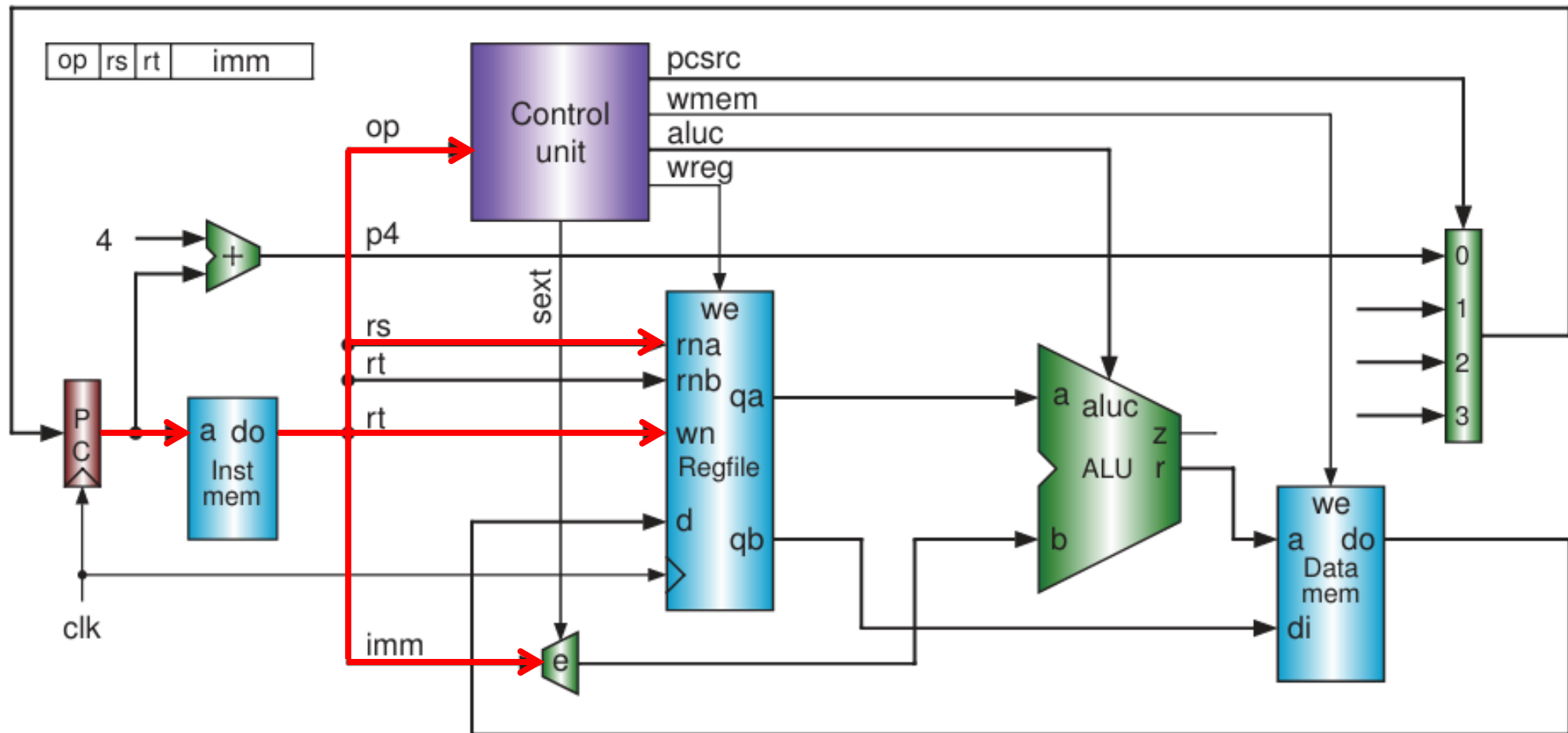
# Single-Cycle CPU Design


- The circuit required by load/store instructions.





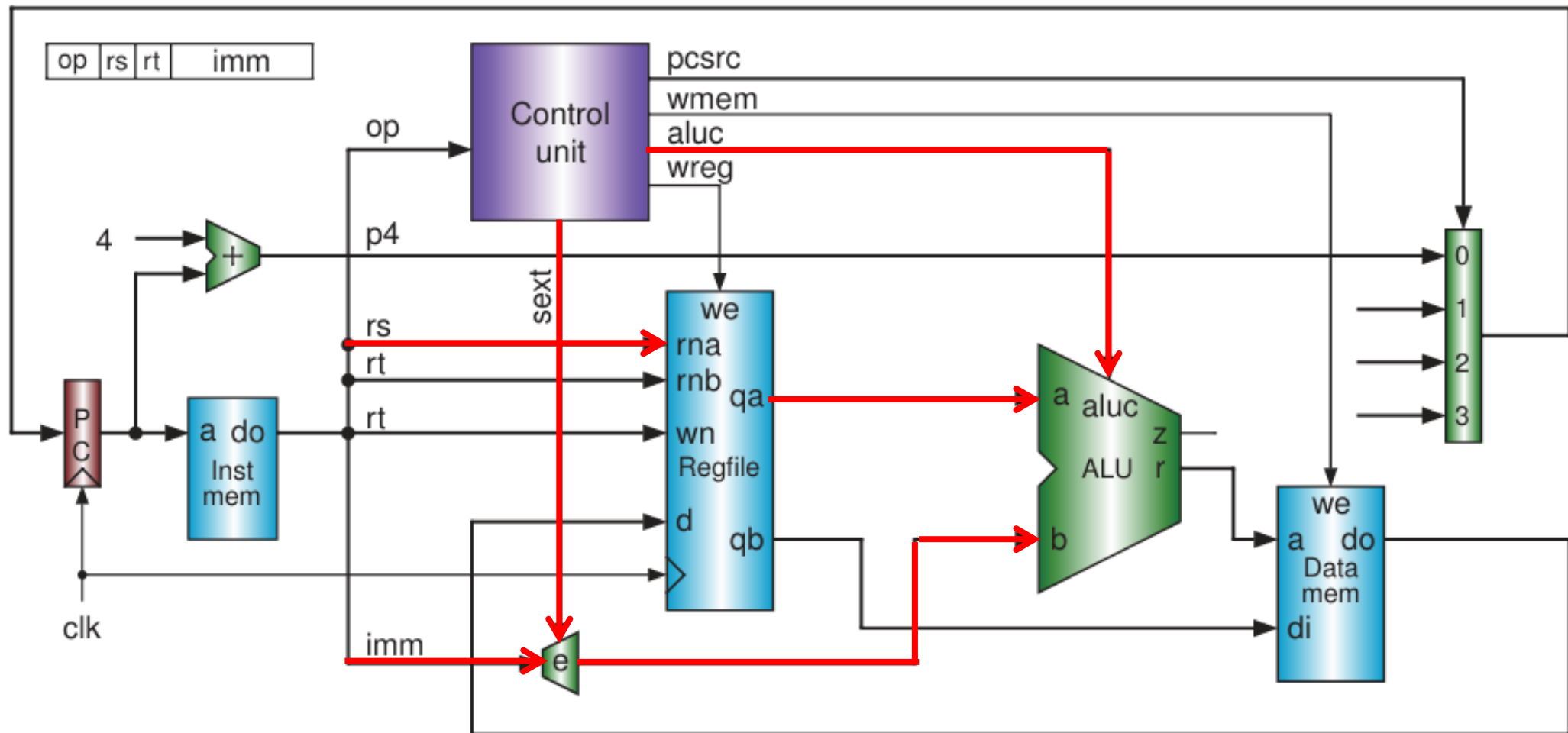
# Single-Cycle CPU Design

- The circuit required by load/store instructions.




# Single-Cycle CPU Design

- */w*

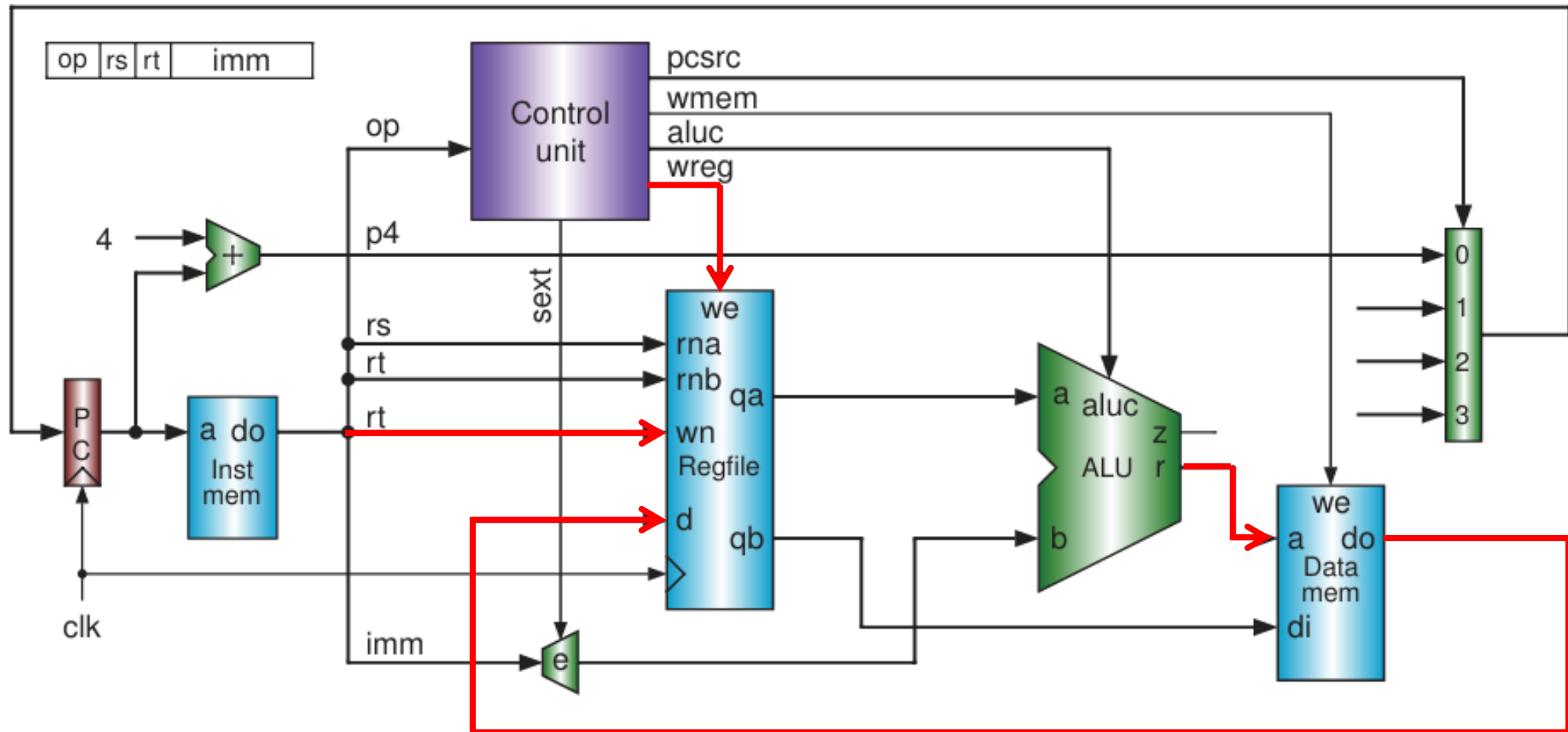


# Single-Cycle CPU Design

## ■ SW

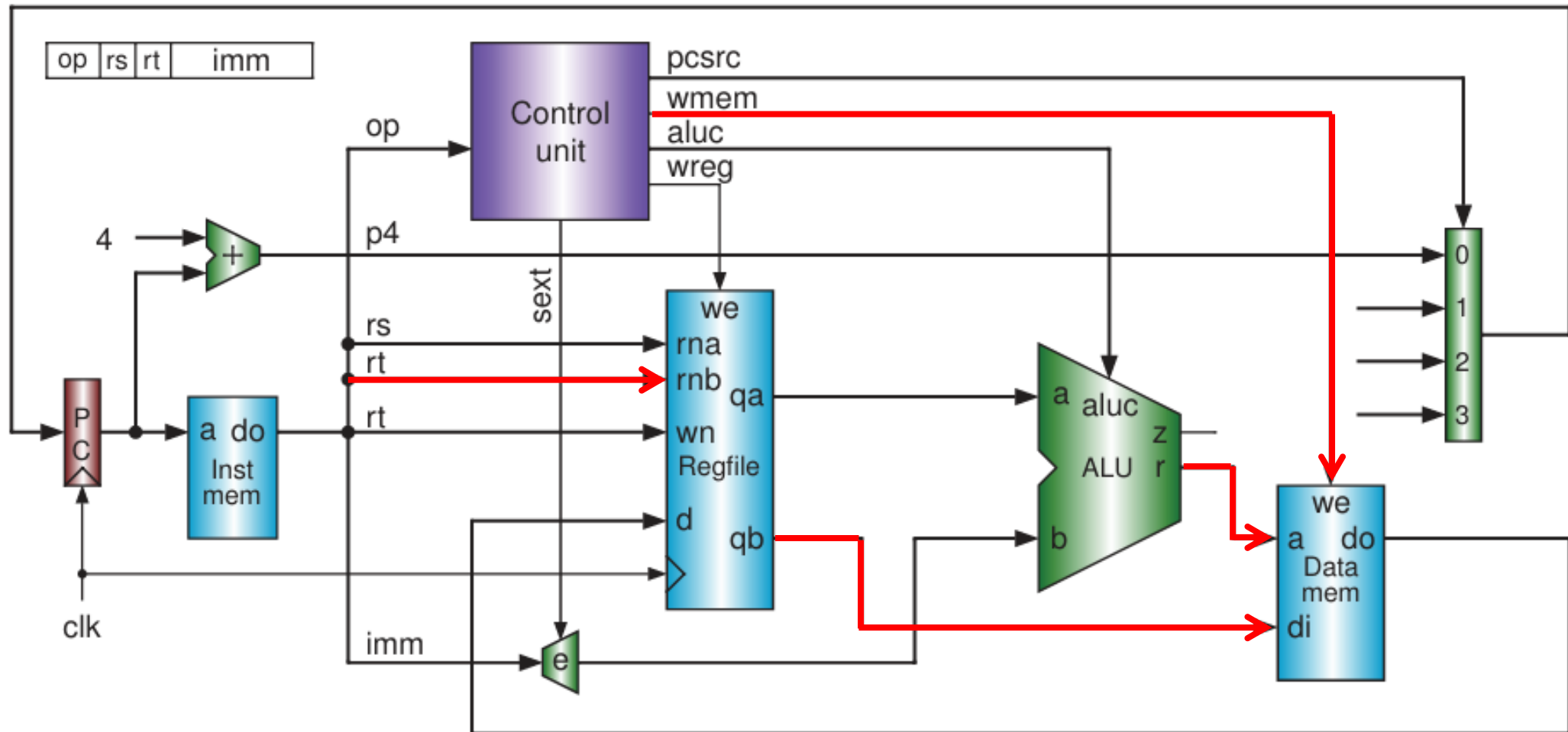

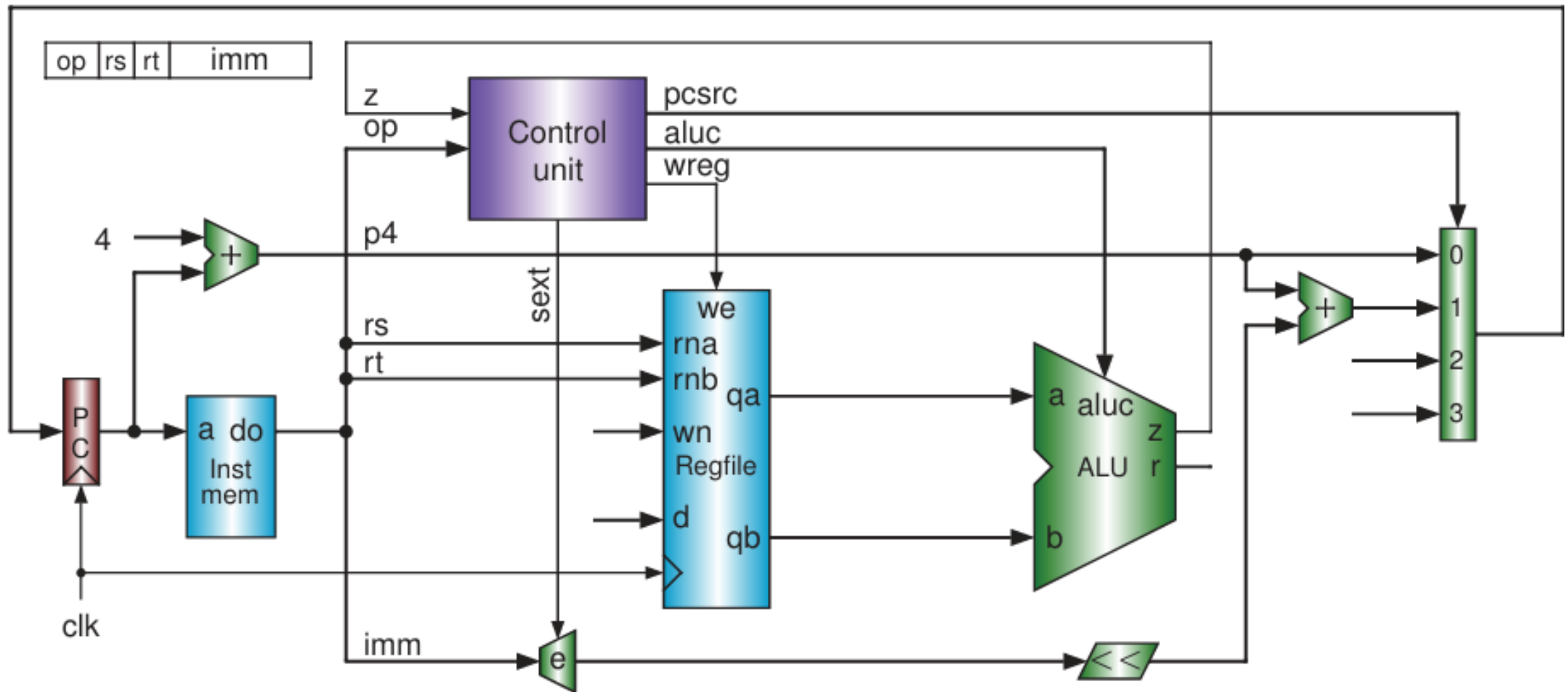
# Single-Cycle CPU Design

- The circuits required by conditional branch instructions.




# Single-Cycle CPU Design

- *beq/bne* (instruction fetch)

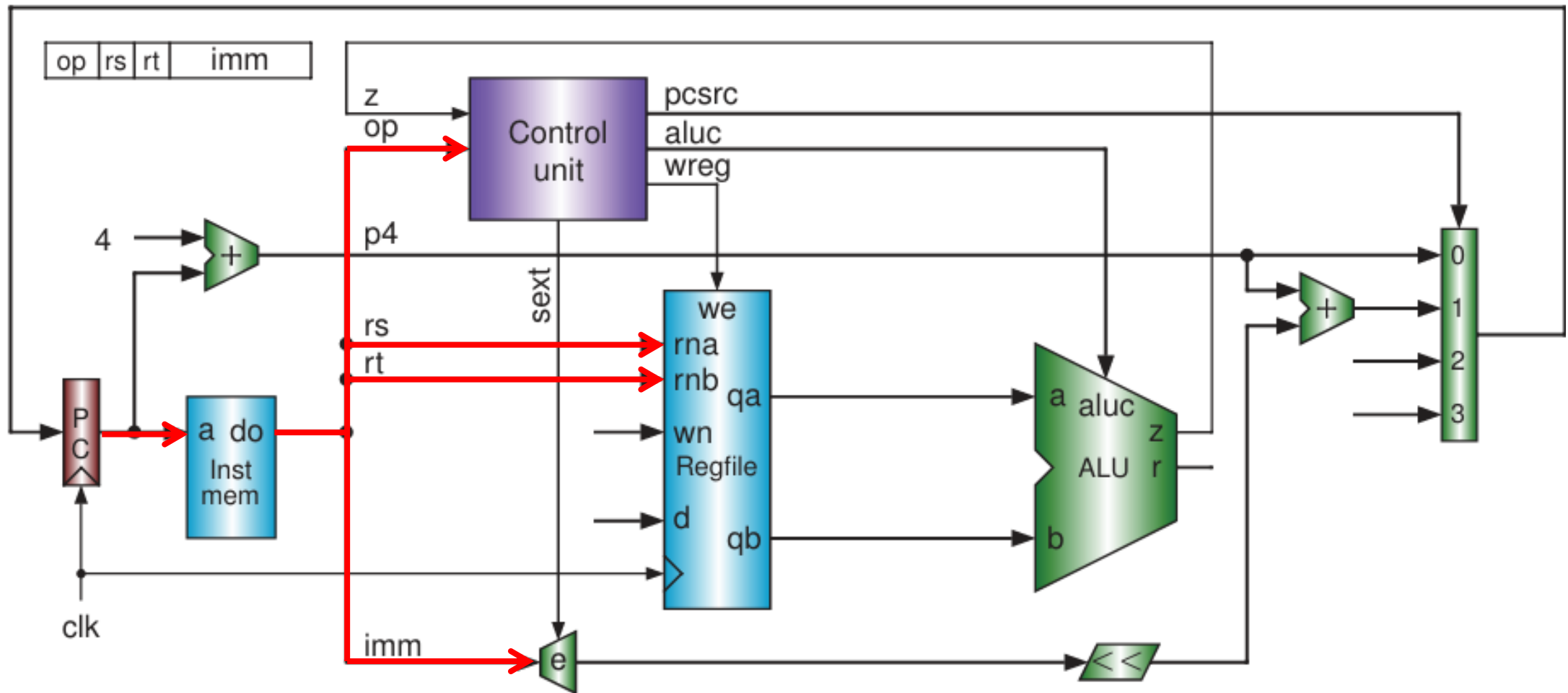


# Single-Cycle CPU Design

- *beq/bne* (instruction execute)

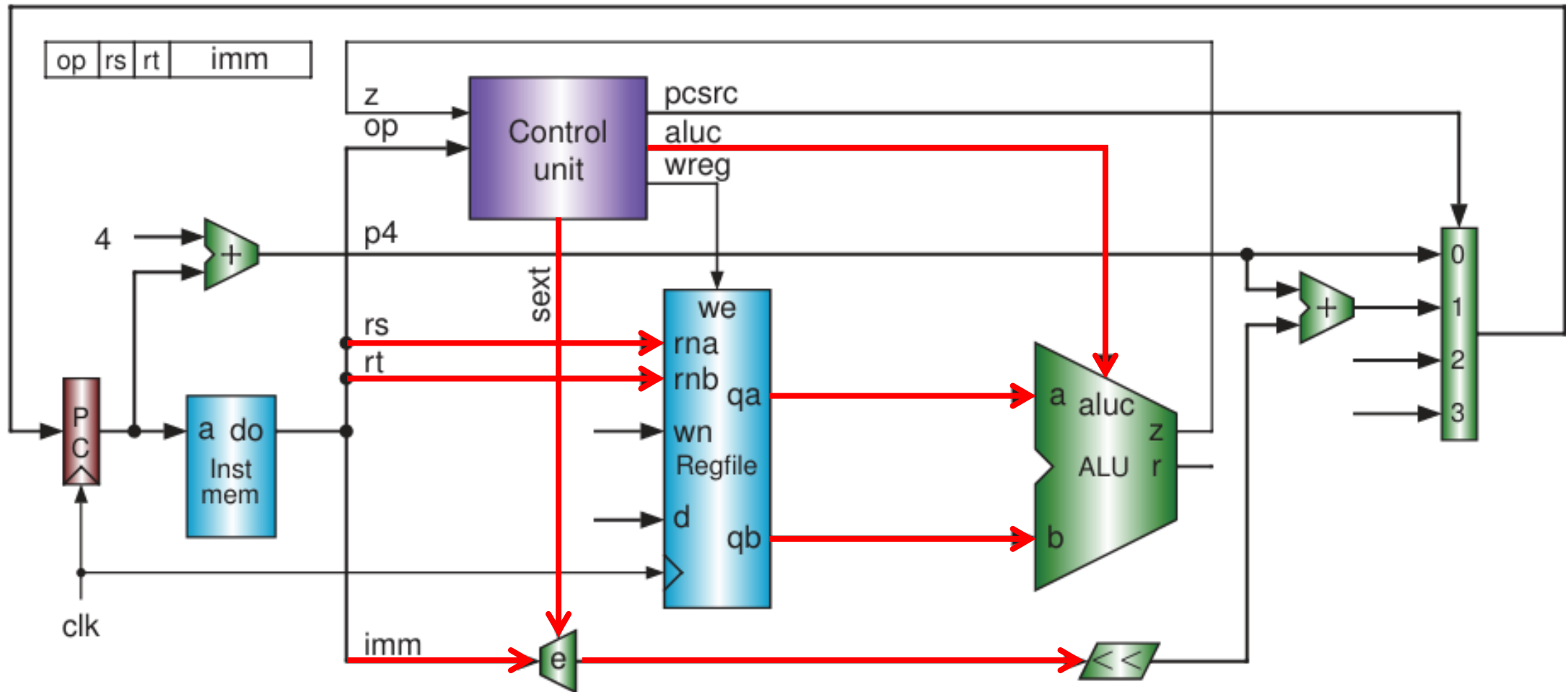


# Single-Cycle CPU Design

- *beq/bne* (comparison result z)

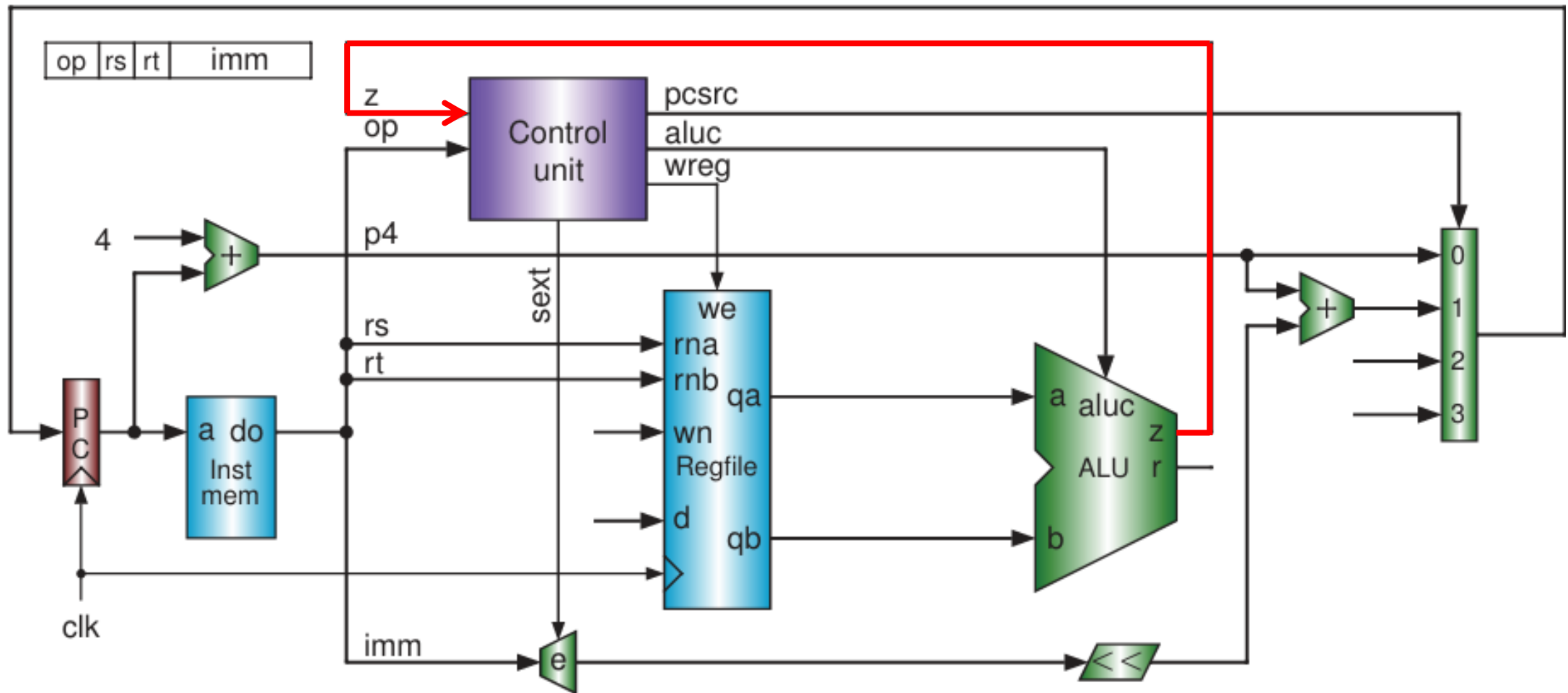

# Single-Cycle CPU Design


- *beq/bne* (branch target address)

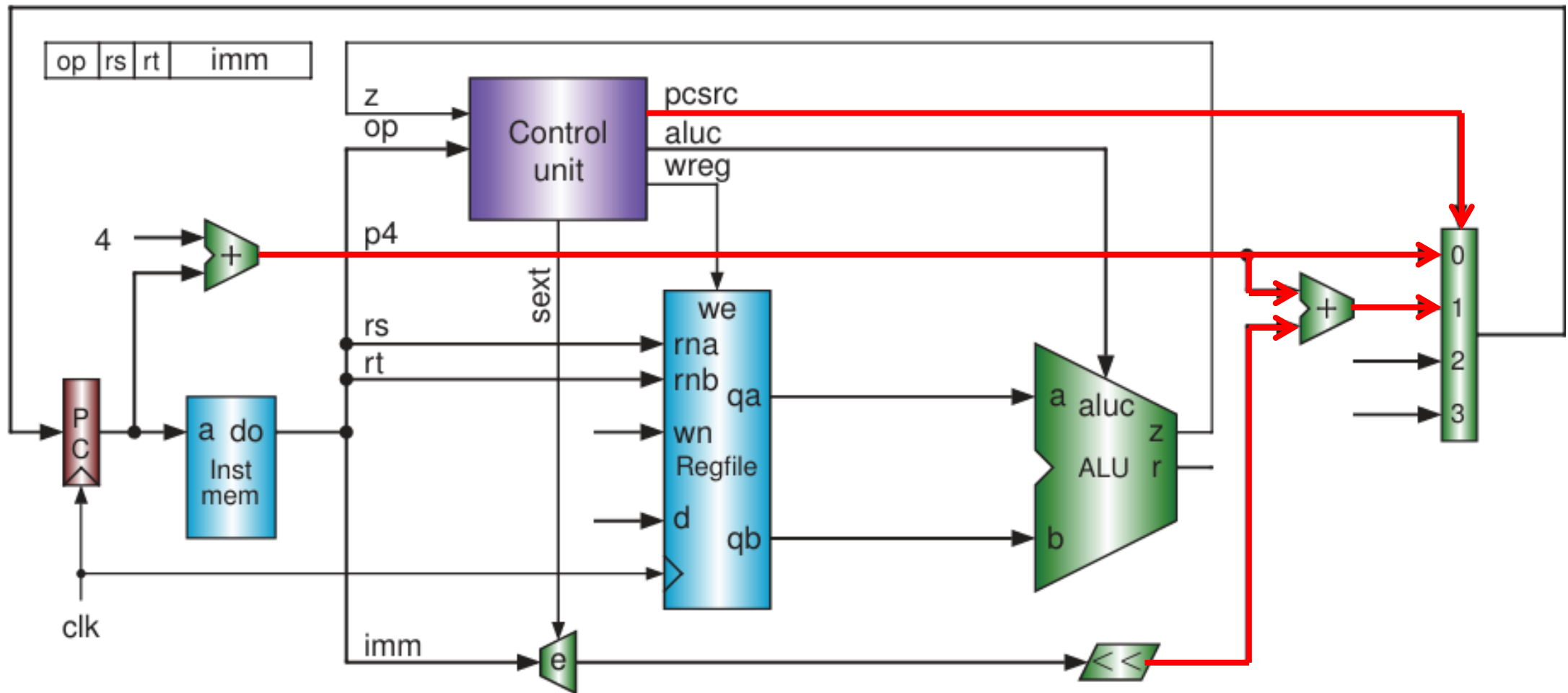




# Single-Cycle CPU Design

- *beq/bne* (branch)

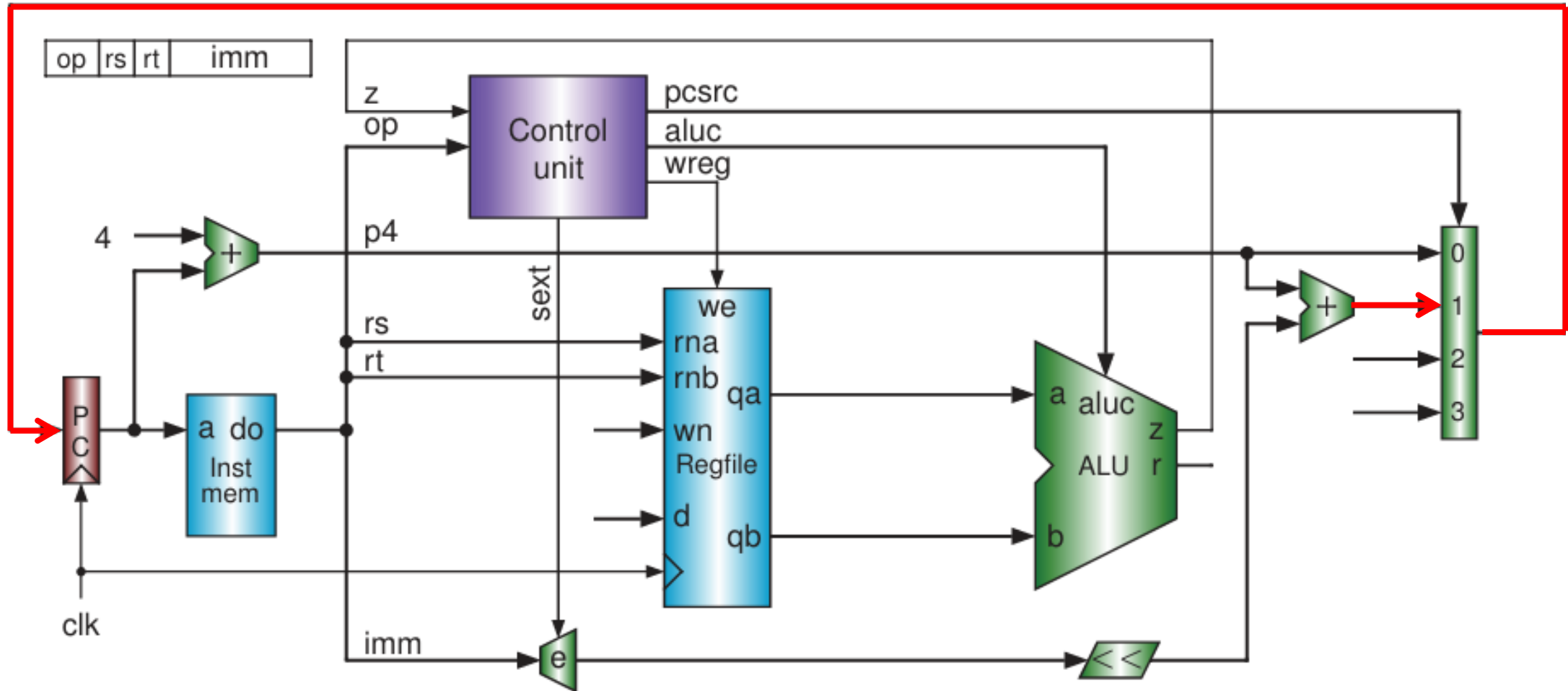


# Single-Cycle CPU Design

- *beq/bne* (branch X)

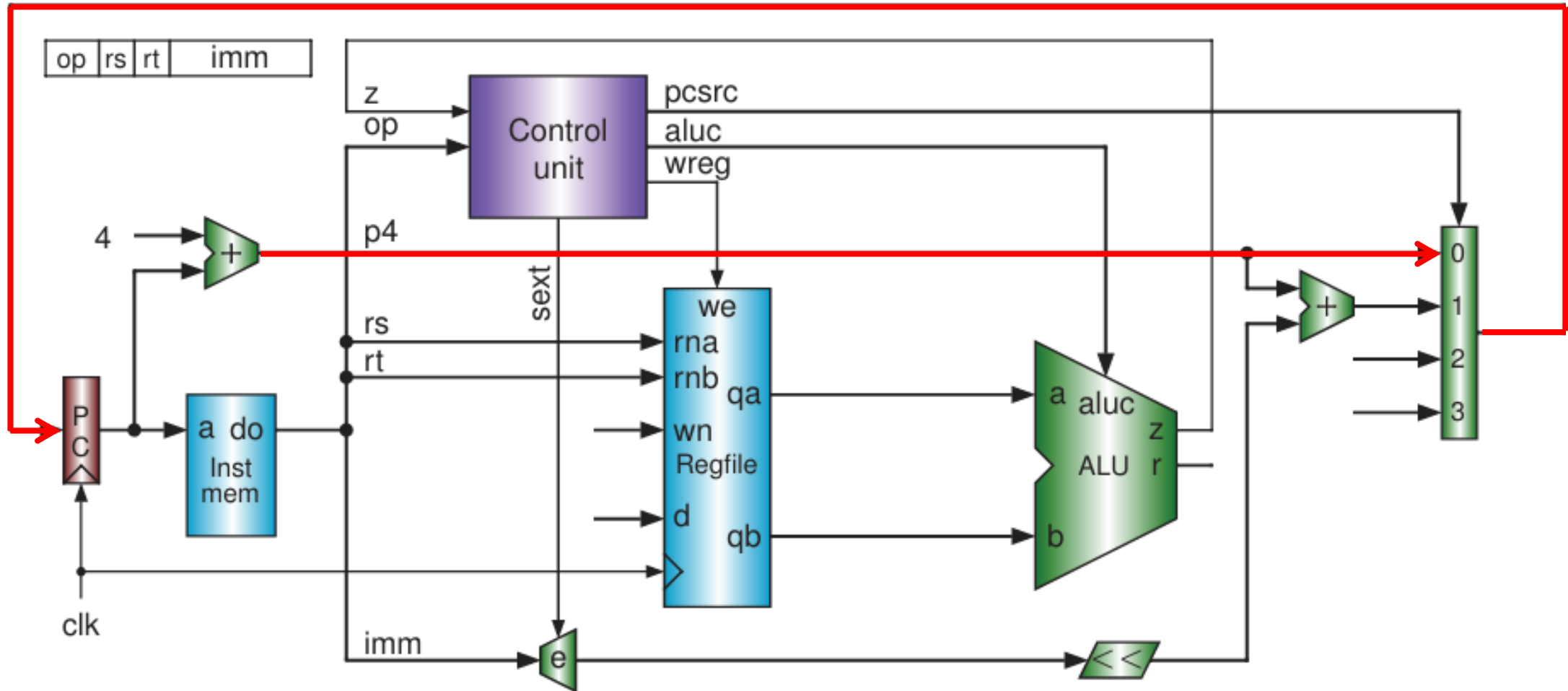

 
# Single-Cycle CPU Design

- The circuits required by J-format instructions.



 
# Single-Cycle CPU Design

- The circuits required by J-format *jal* instructions.



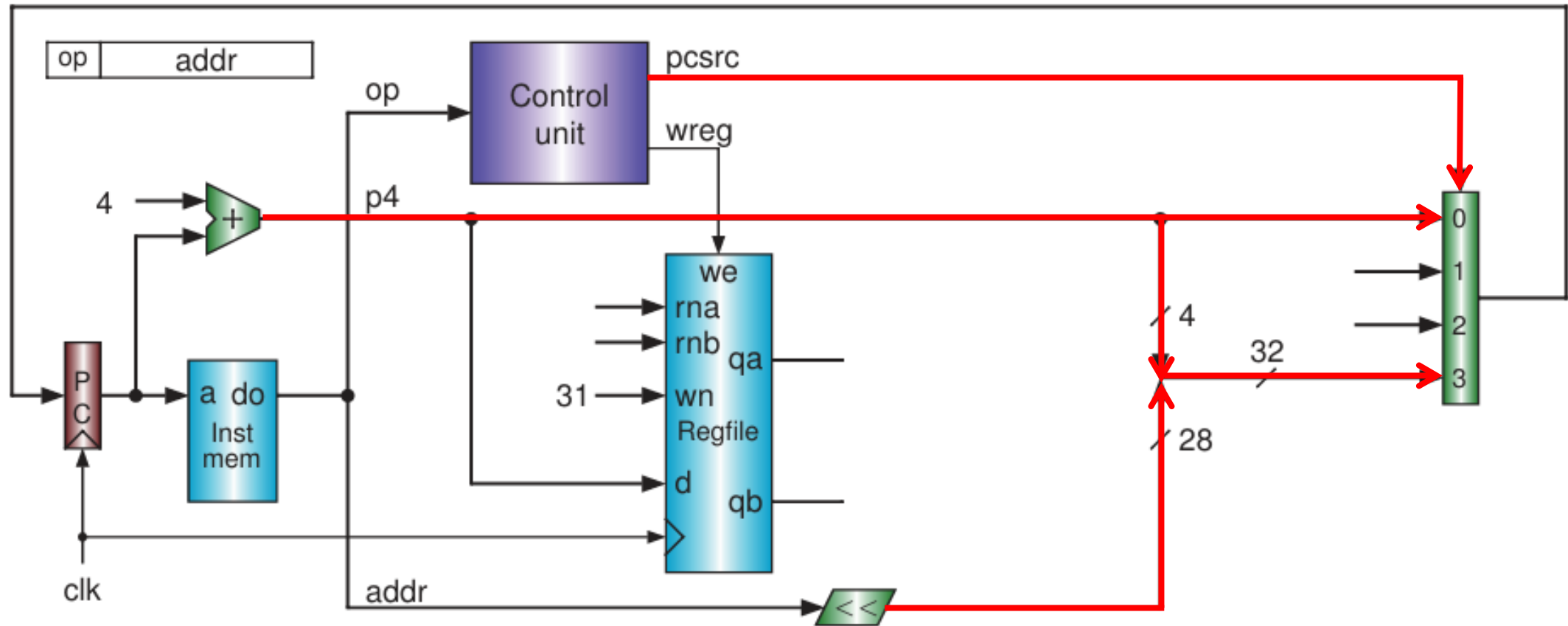
# Single-Cycle CPU Design

- The circuits required by J-format *j/jal* instructions.



 
# Single-Cycle CPU Design

- The circuits required by J-format *j/jal* instructions.



 
# Single-Cycle CPU Design

- The circuits required by R-format *jump-register* instructions.


 
# Single-Cycle CPU Design


- The circuits required by R-format *jump-register* instructions.





 
# Single-Cycle CPU Design

- The circuits required by R-format *jump-register* instructions.



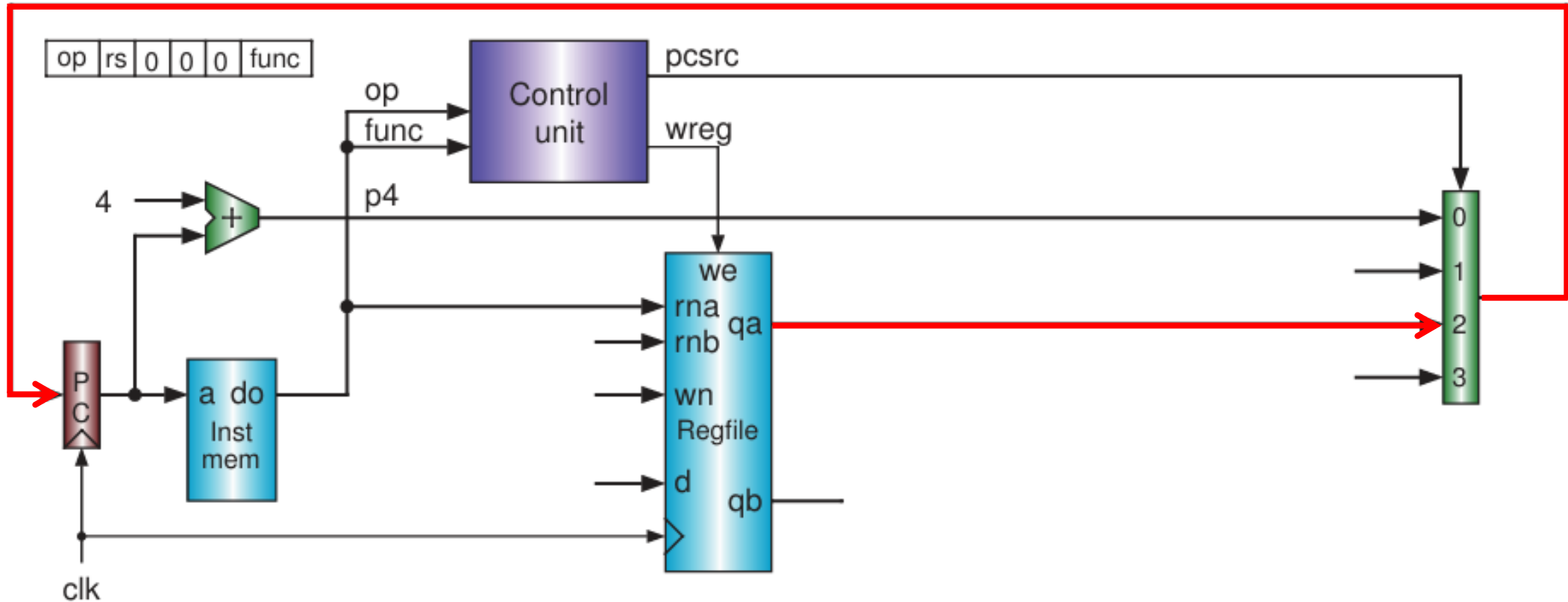
# Single-Cycle CPU Design


- The circuits required by R-format *jump-register* instructions.



# ALU

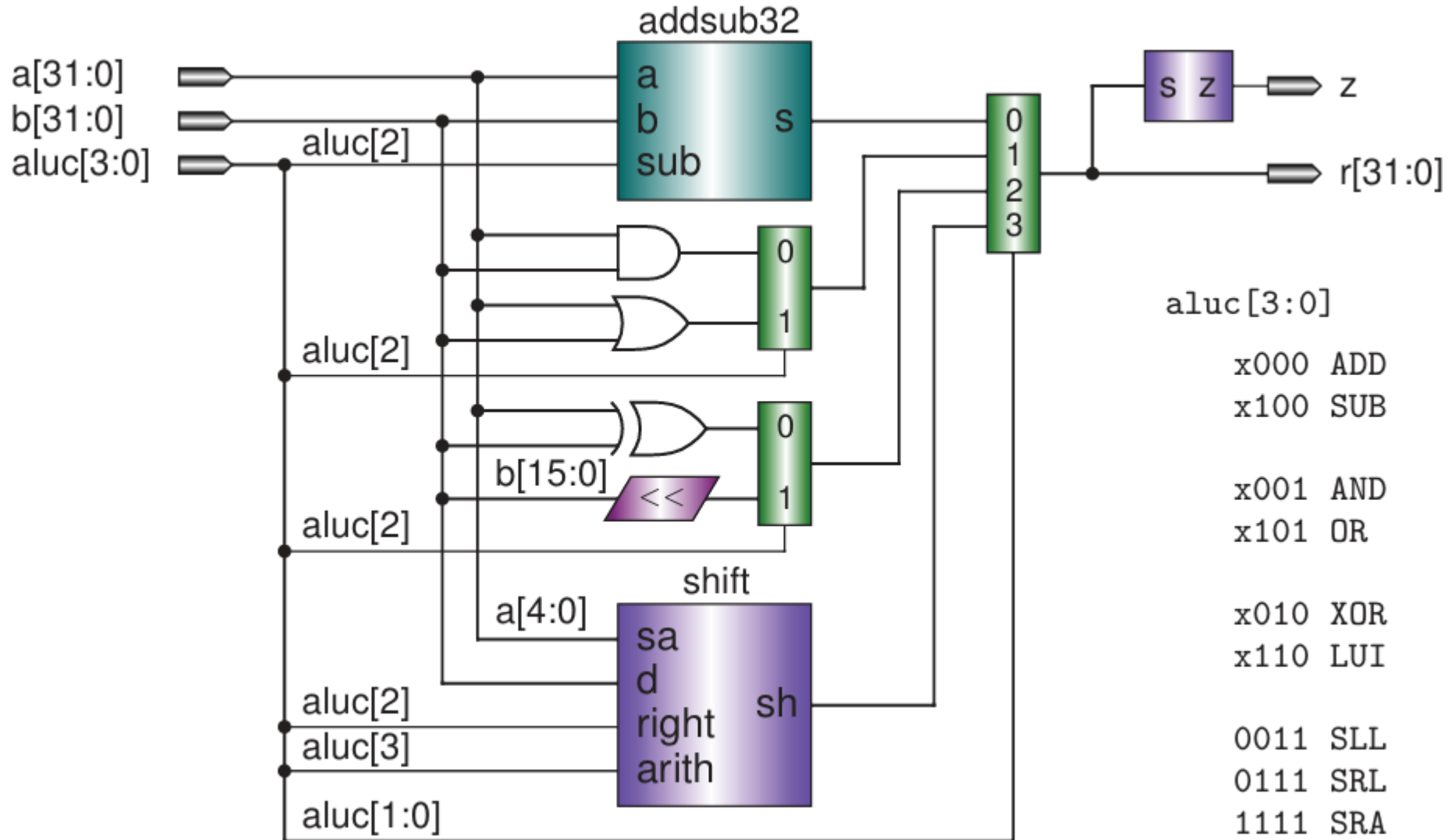


# ALU

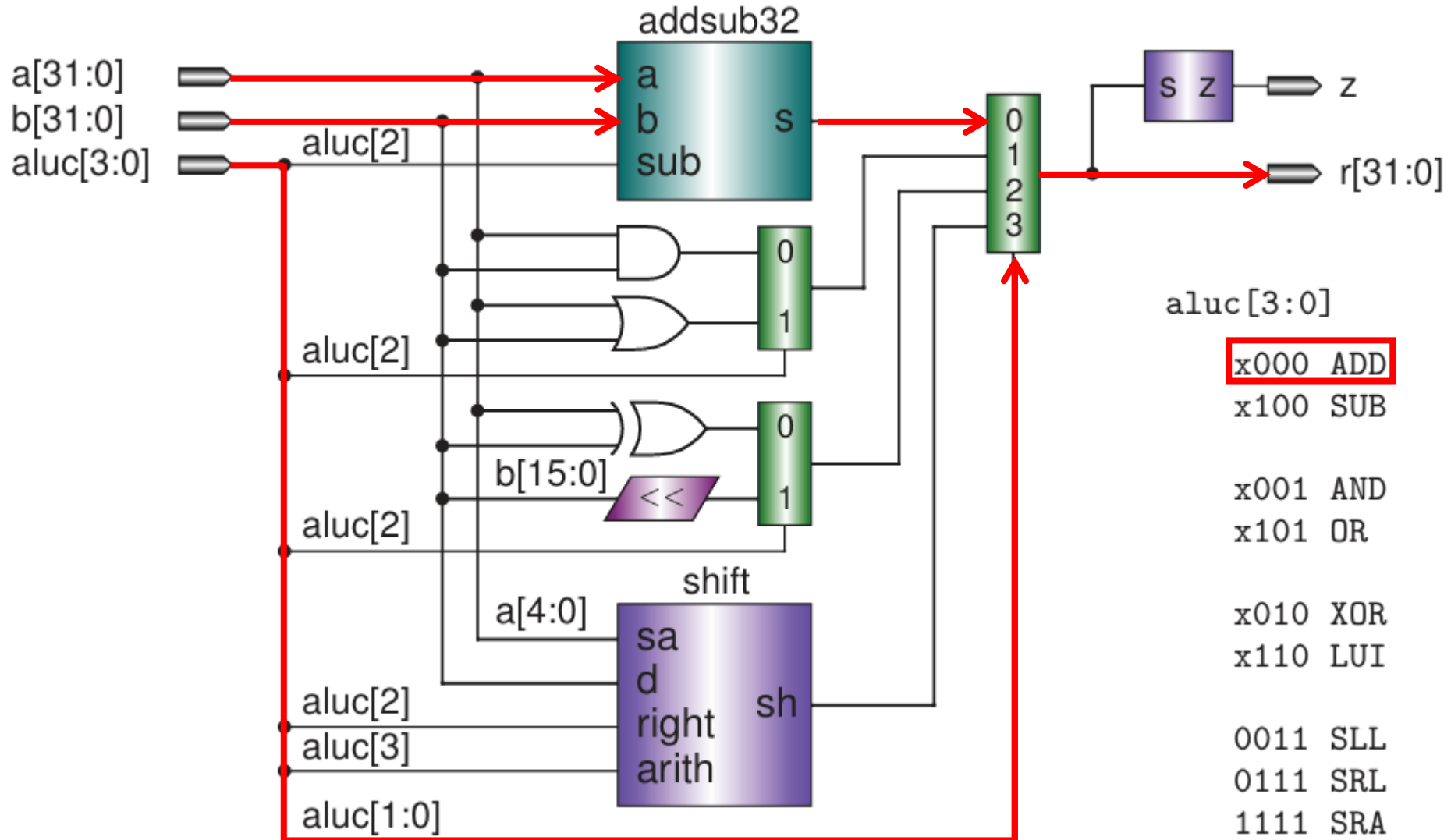





# ALU

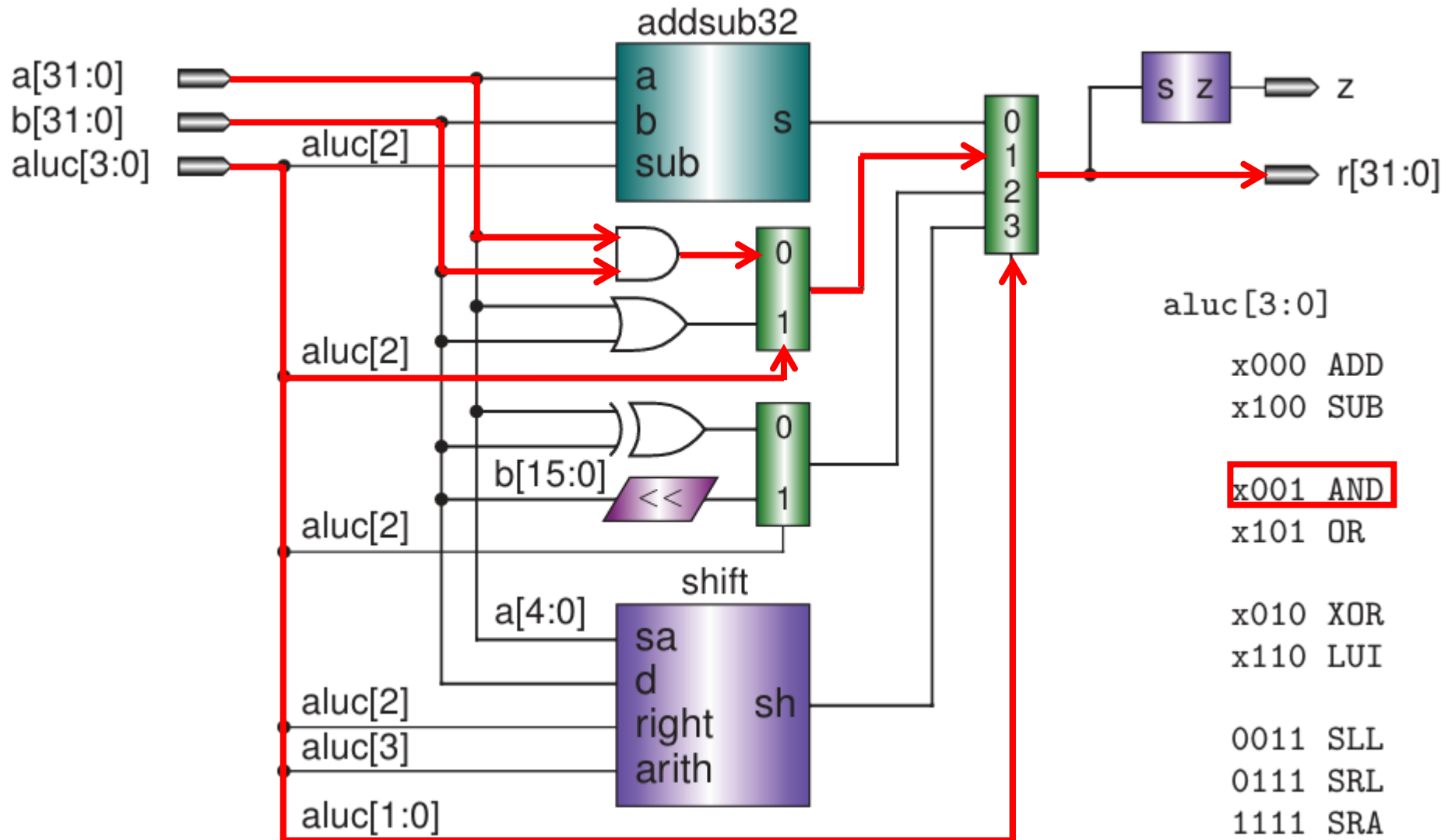

# ALU

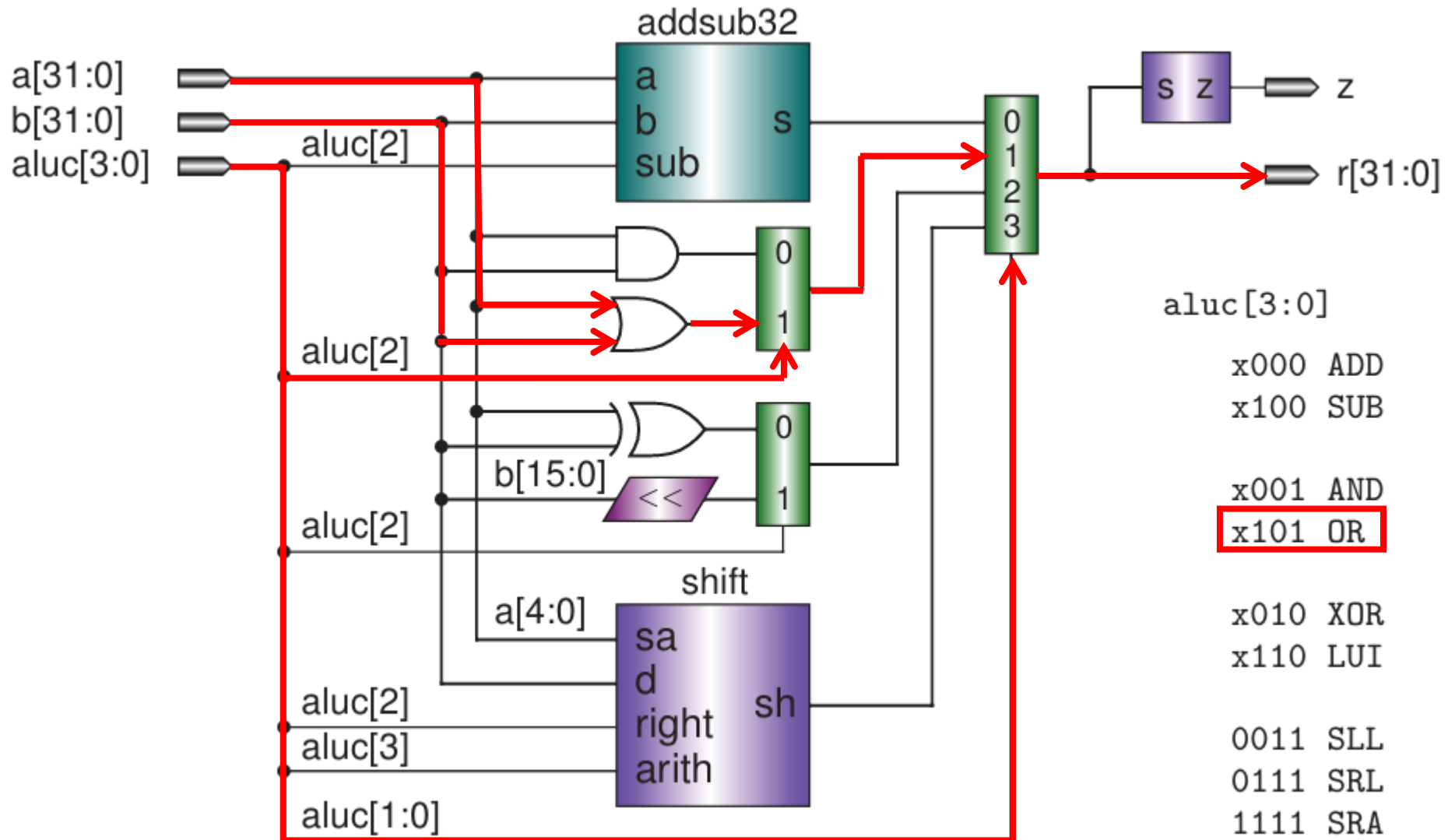


# ALU

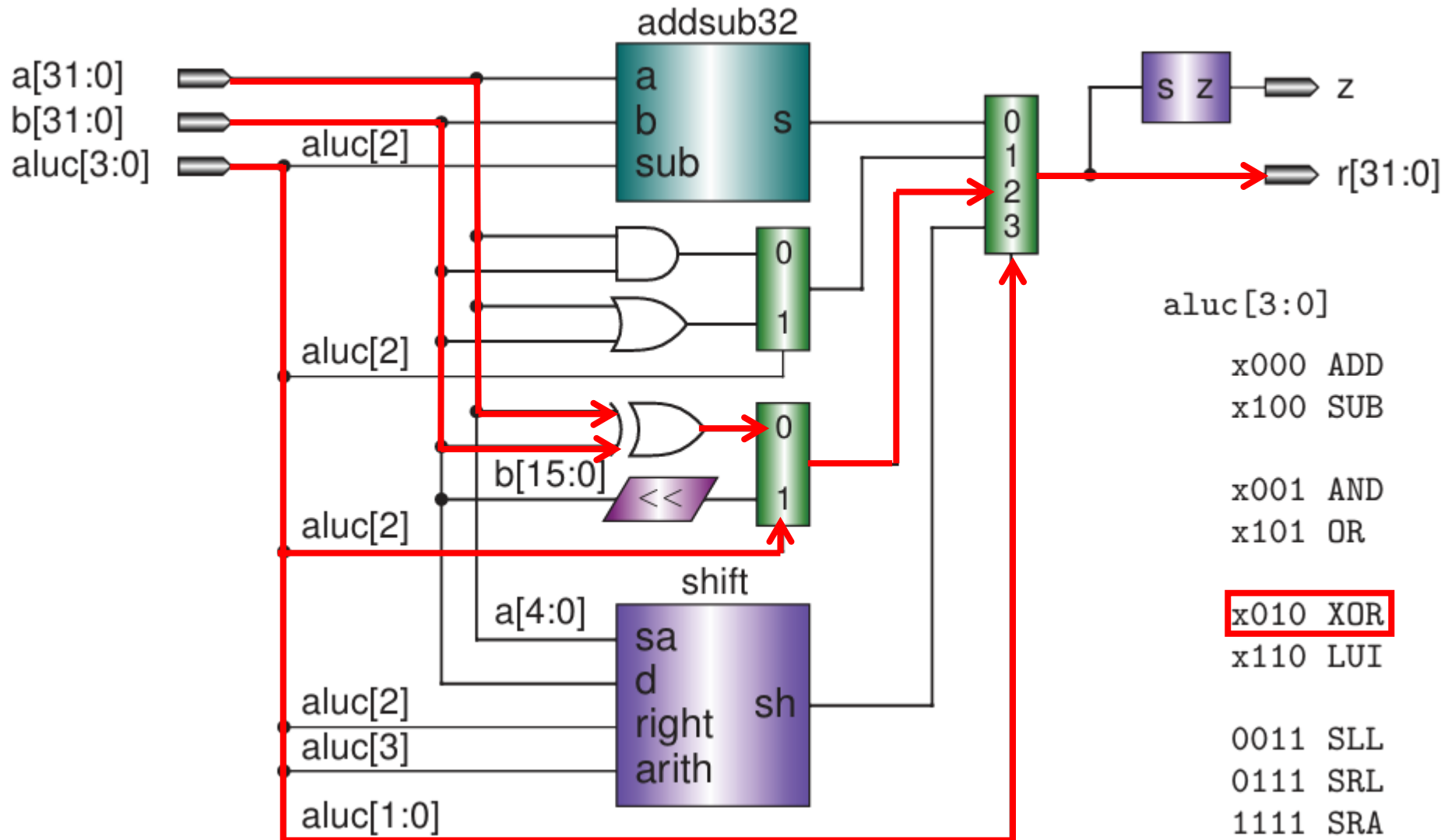





# ALU

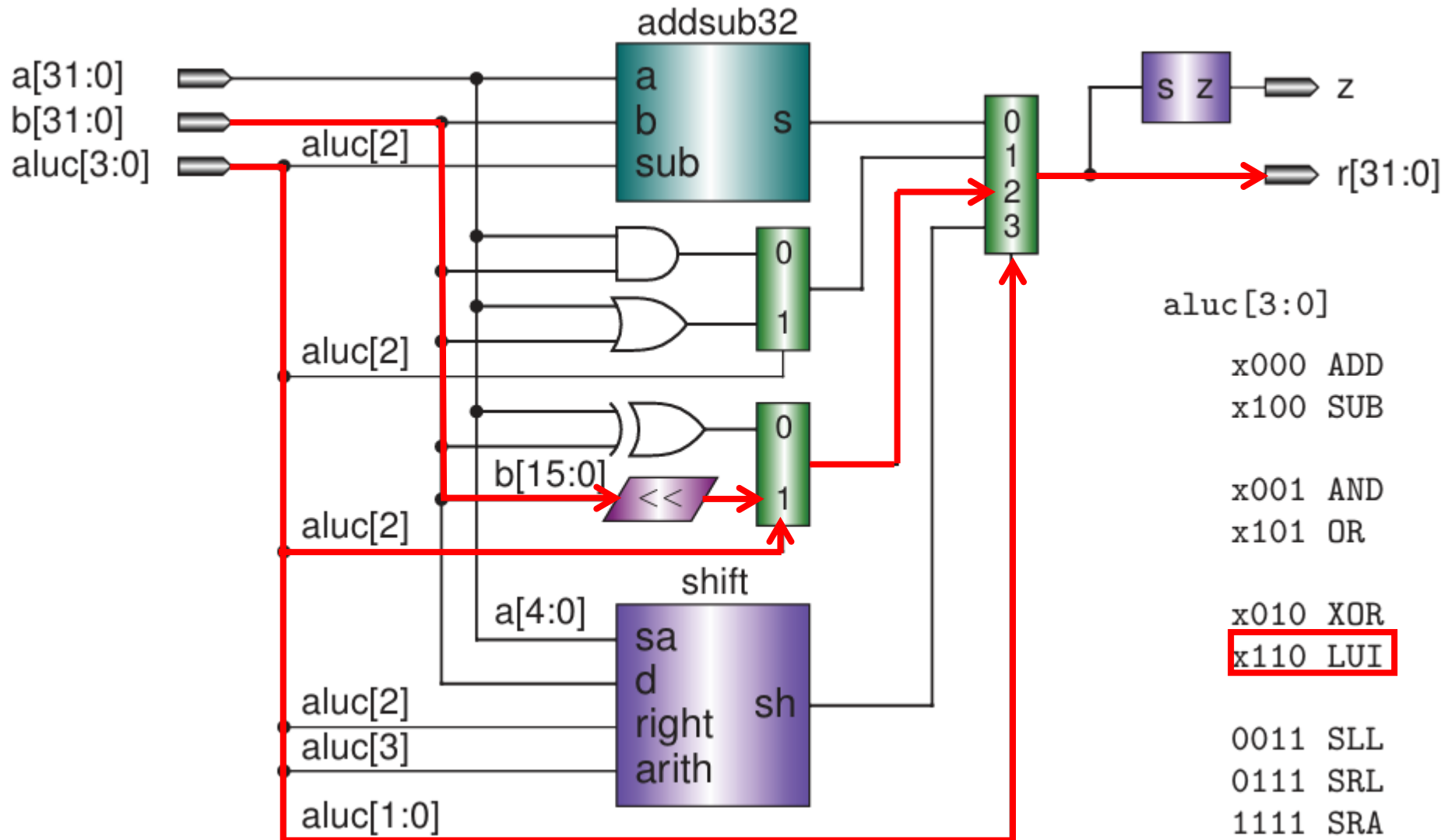

# ALU

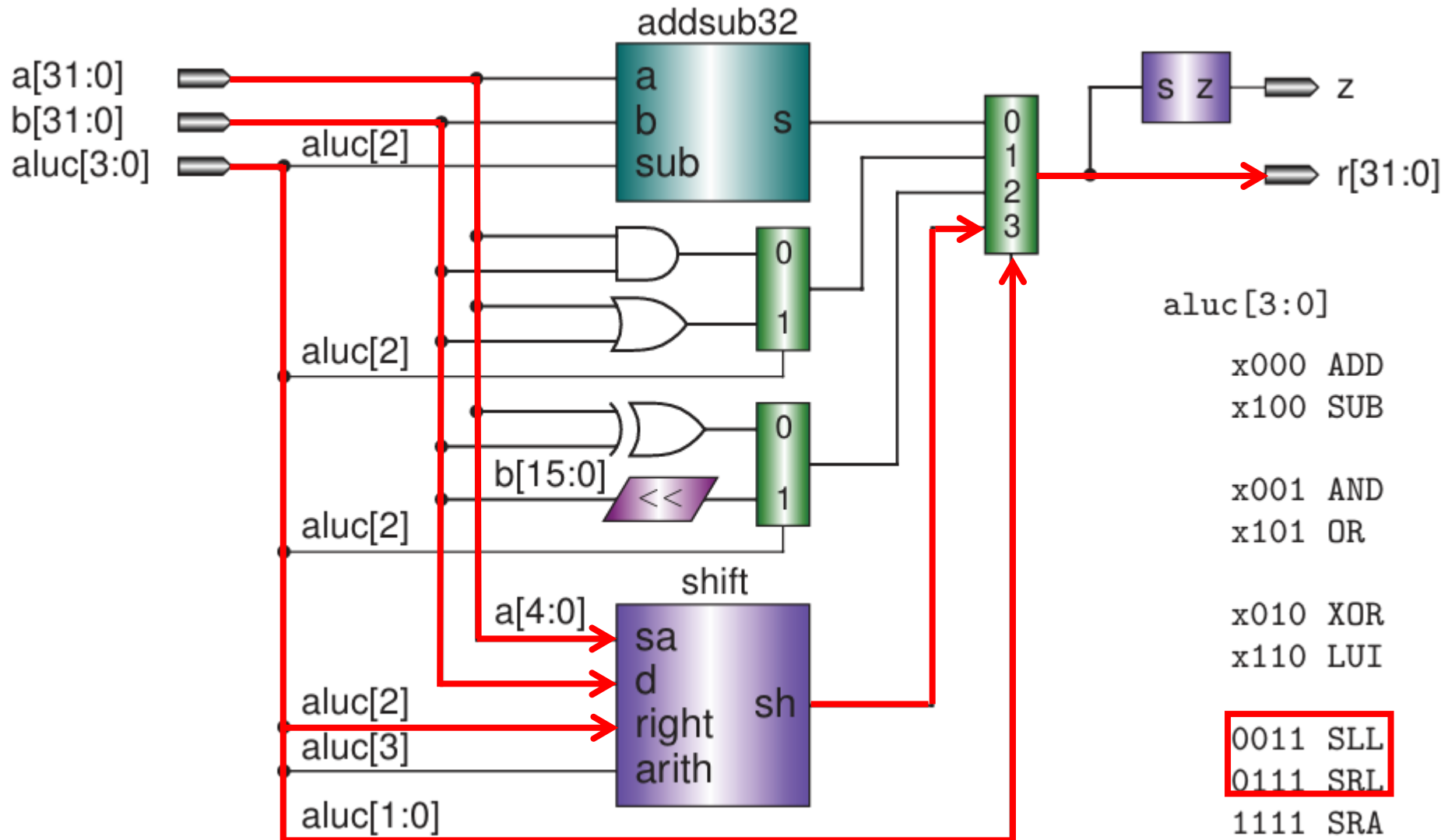


# ALU

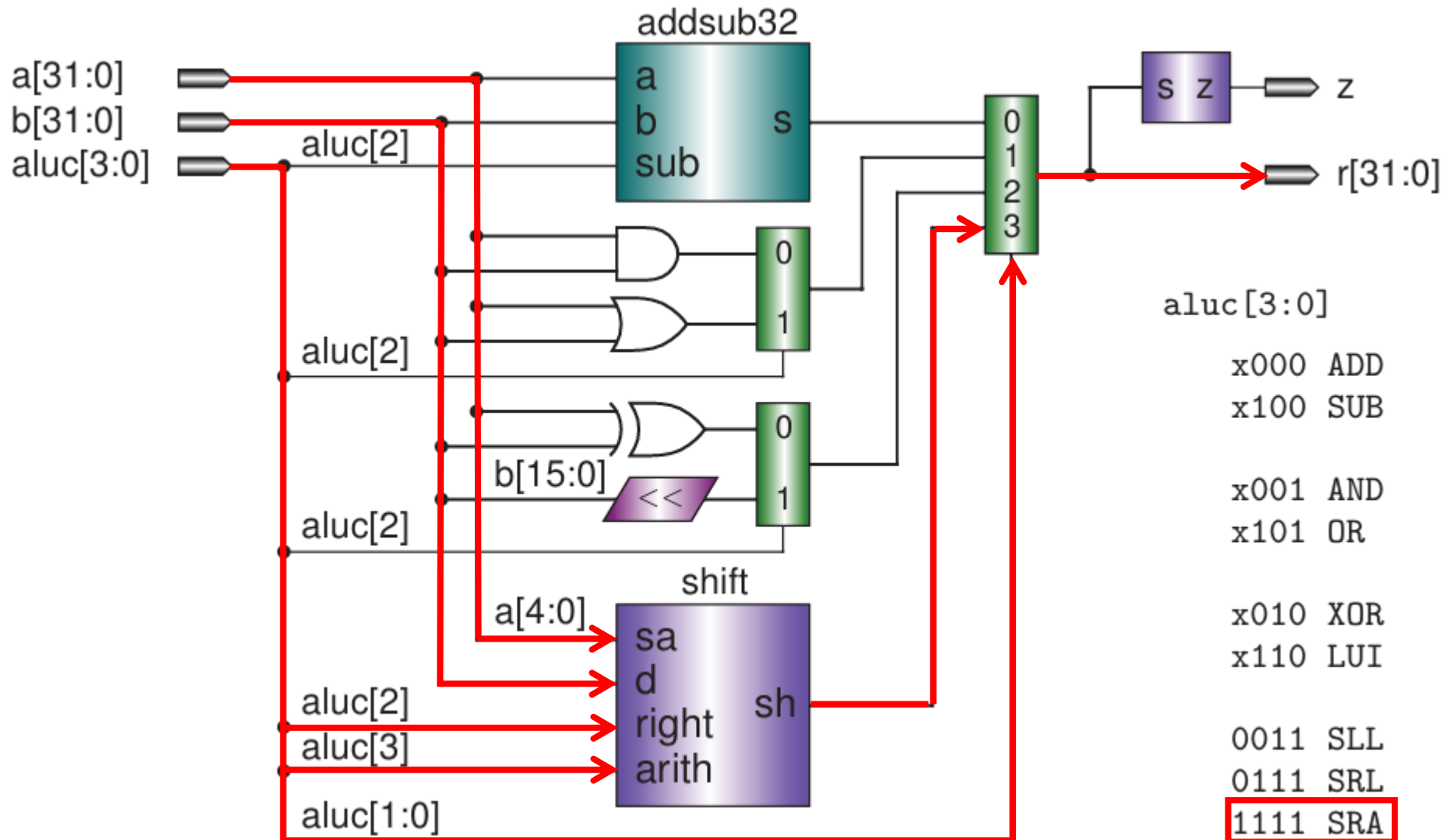

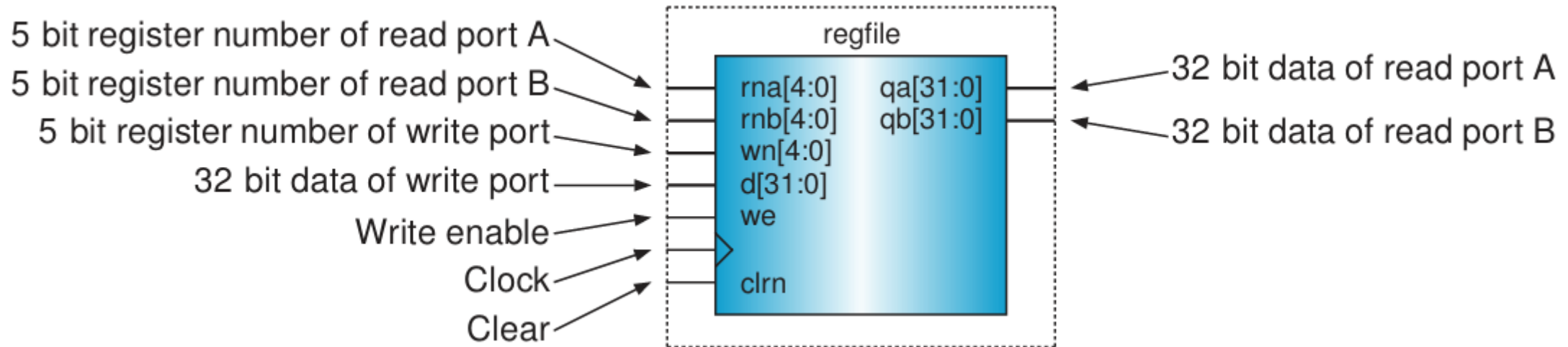
# Register File

- The register file contains 32 general-purpose registers.
- Two read ports (port A and B) and write port.
- Each port has a 5-bit address input (register number).
- 32-bit data input and write enable are provided for write port.


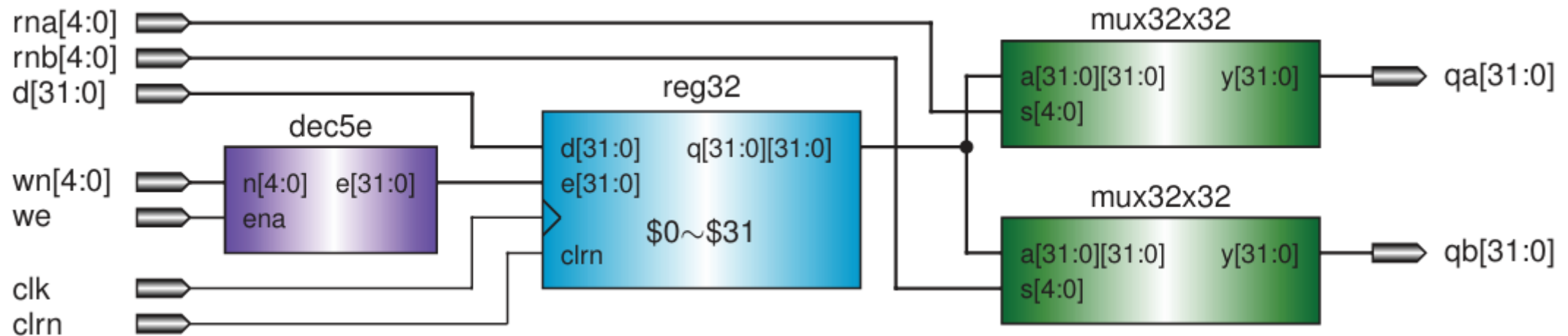
# Register File

- A register file (RF) has 32 bits, it can be designed with 32 D-FFs.
- Each read port uses a 32-bit 32-to-1 MUX to select one register output according to its 5-bit read register number.



# Datapath

---

- A CPU is consists of a **datapath** and a **control unit**.
- A **datapath** is a collection of functional units.
  - ✓ ALU, register file, and MUX
- A **control unit** manages the operations of the **datapath**.

# Next PC

- Selection for Next PC (Selection Signal: *pcsrc*)
- The PC will be updated on the rising edge of the clock.
- PC+4 will be written to the PC.
- But *beq/bne, jr, j/jal* may transfer control to a branch or jump target address not PC+4
- 4-to-1 MUX can be used to select an address for the next PC.

`beq/bne rs, rt, label # if (eq/ne) pc <-- label`

op	rs	rt	offset
----	----	----	--------


`jr rs # pc <-- rs`

op	rs	0	0	0	func
----	----	---	---	---	------

`j/jal address # pc <-- address << 2`


op	address
----	---------

# Next PC

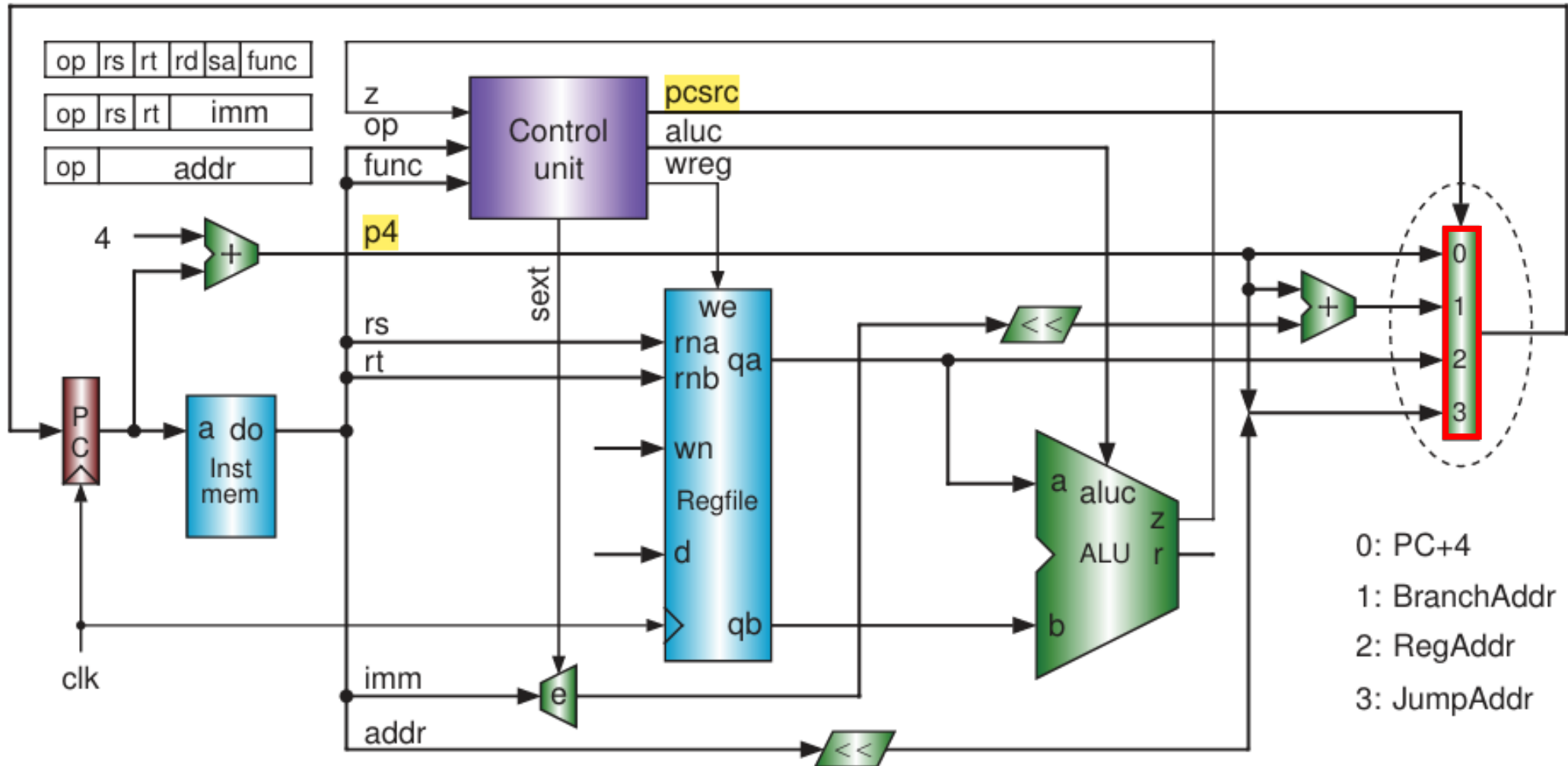





# Next PC

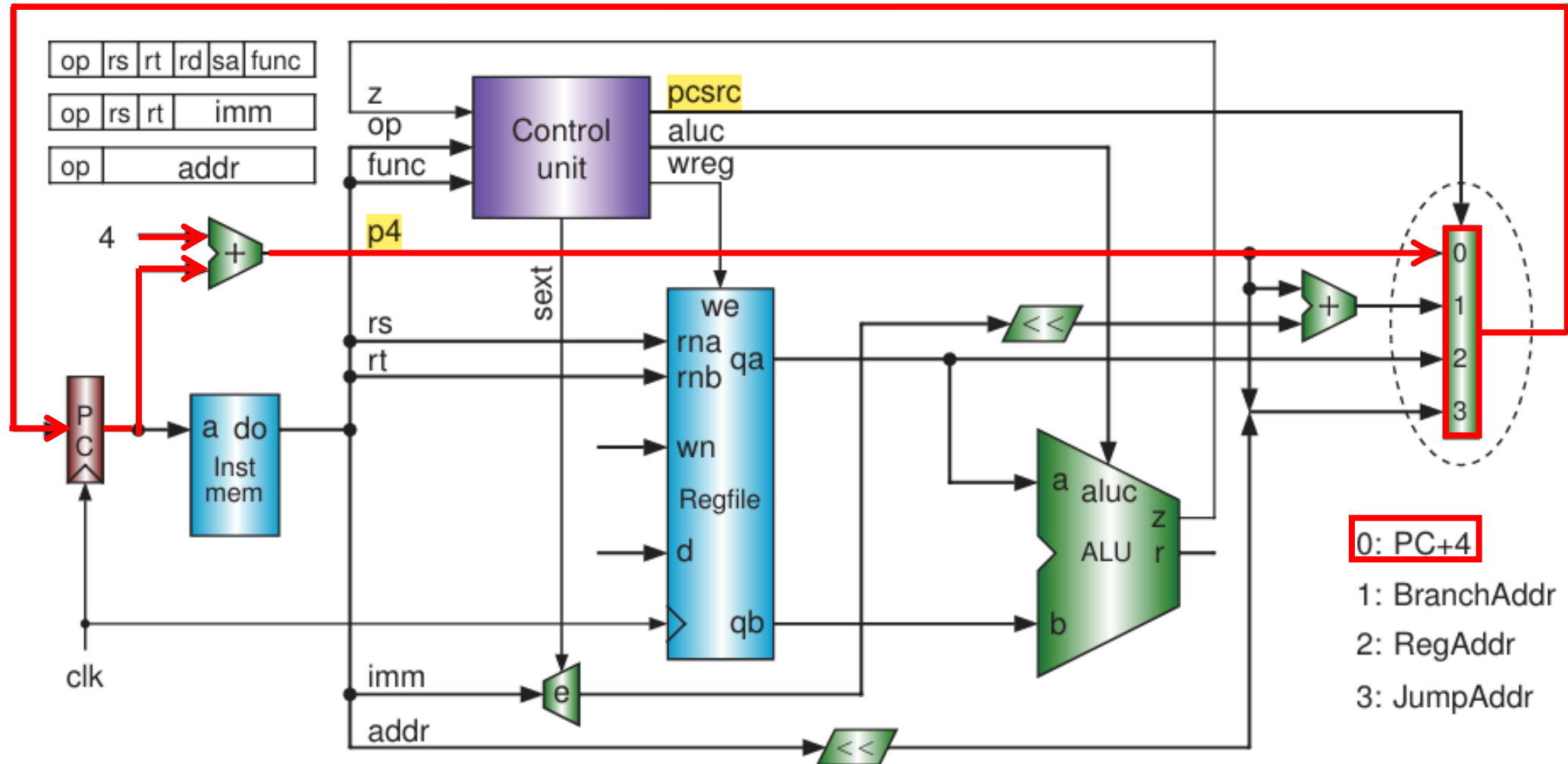


# Next PC

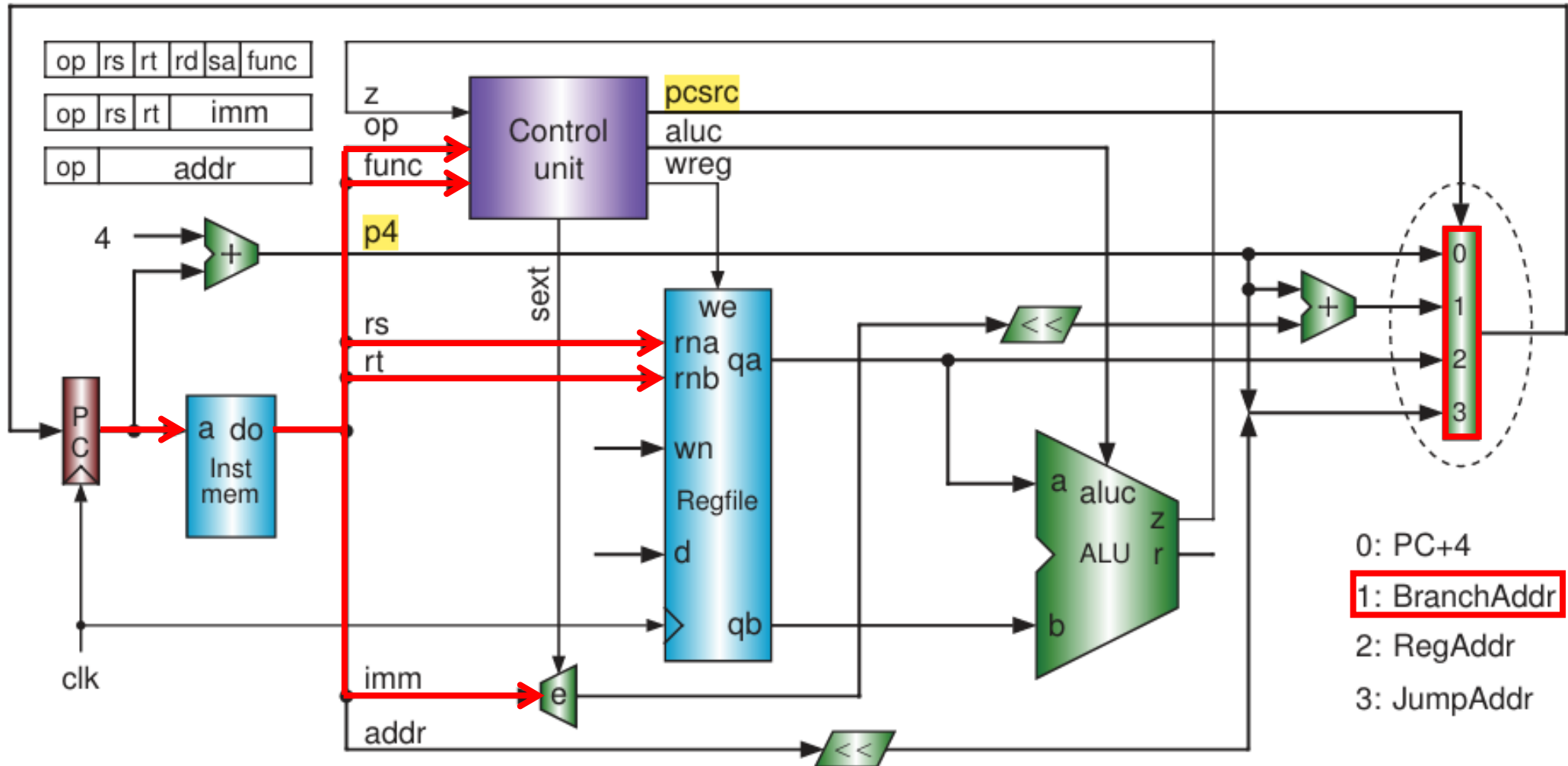


# Next PC

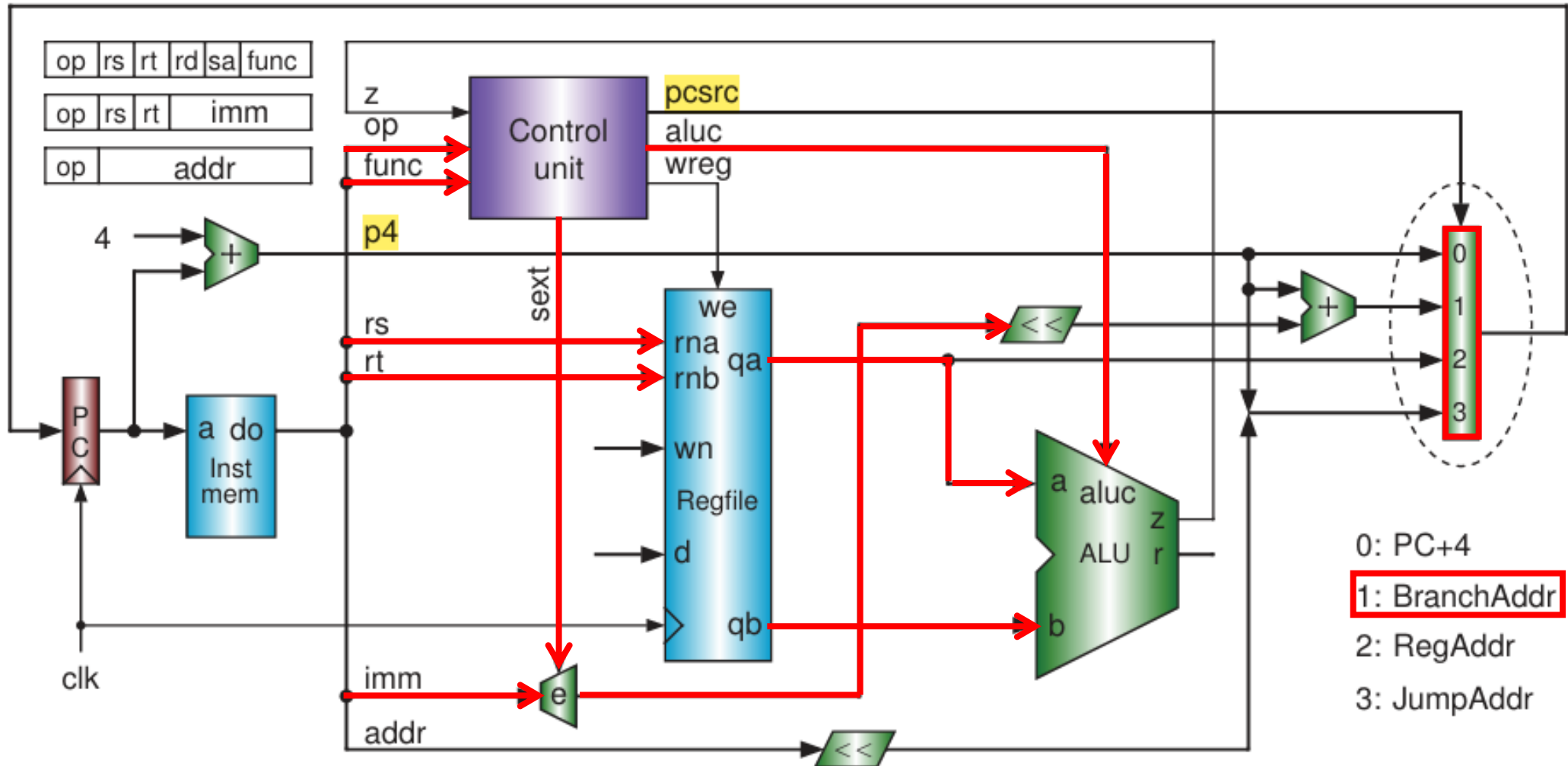


# Next PC

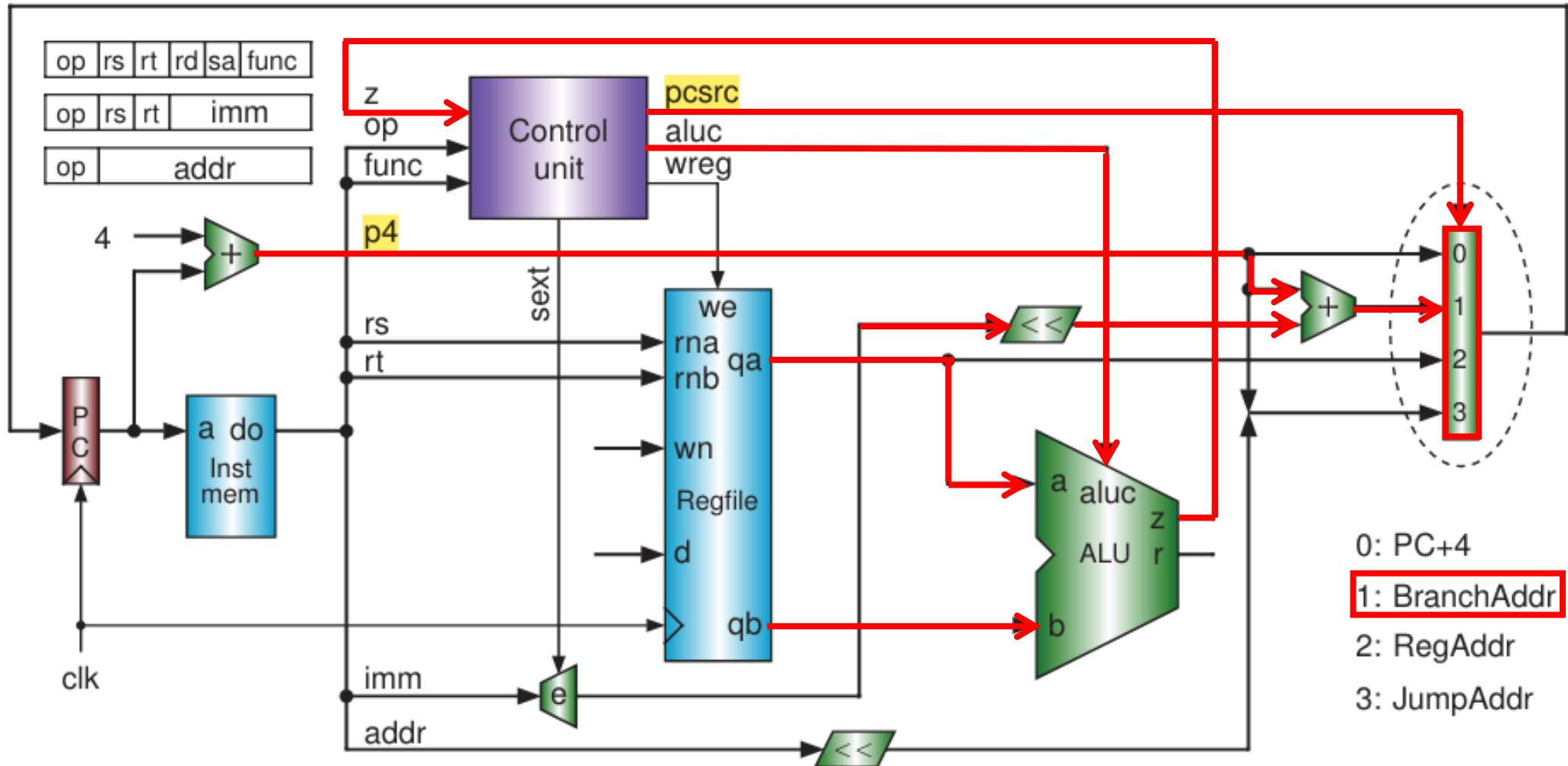


# Next PC

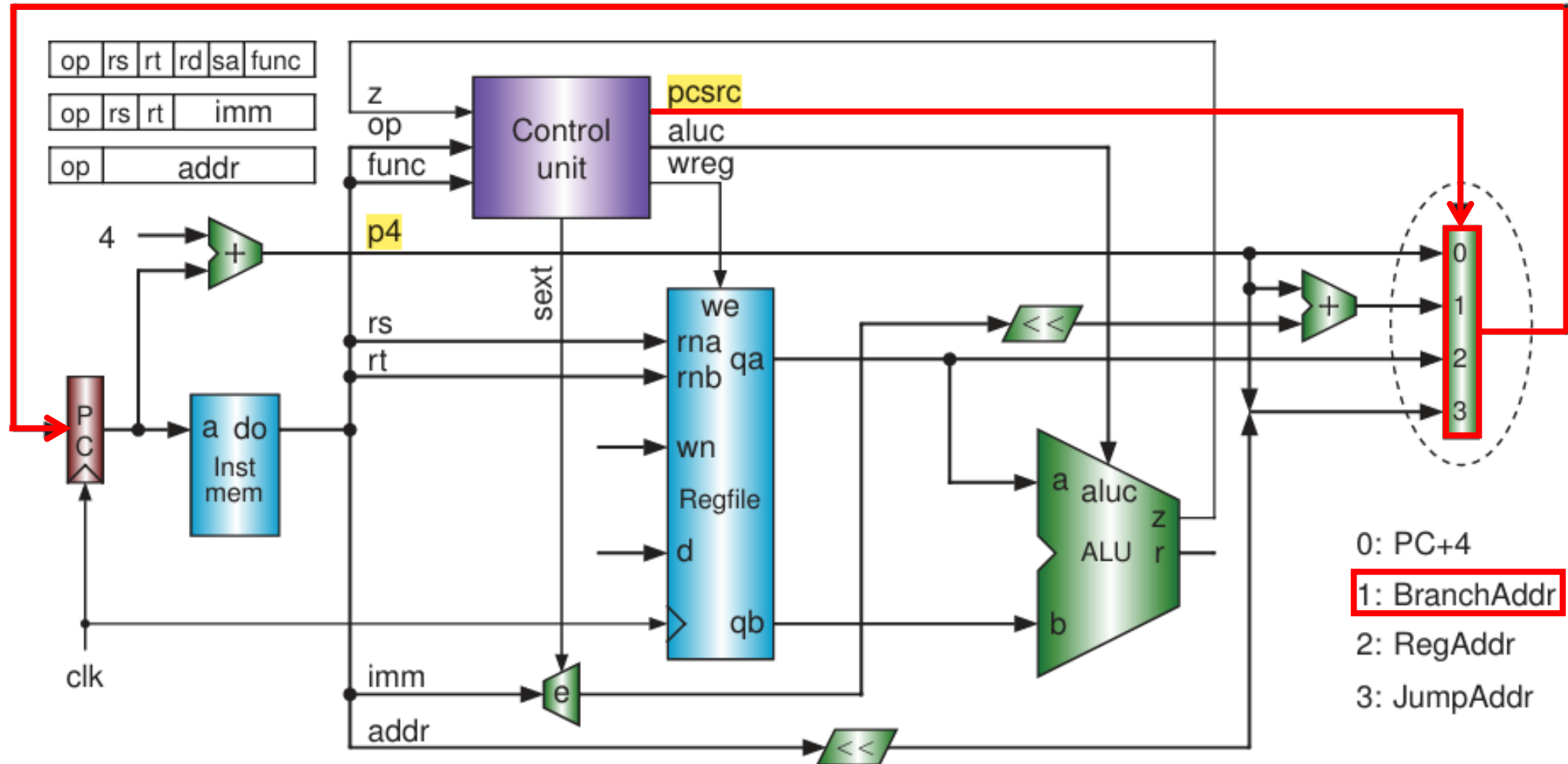

# Next PC

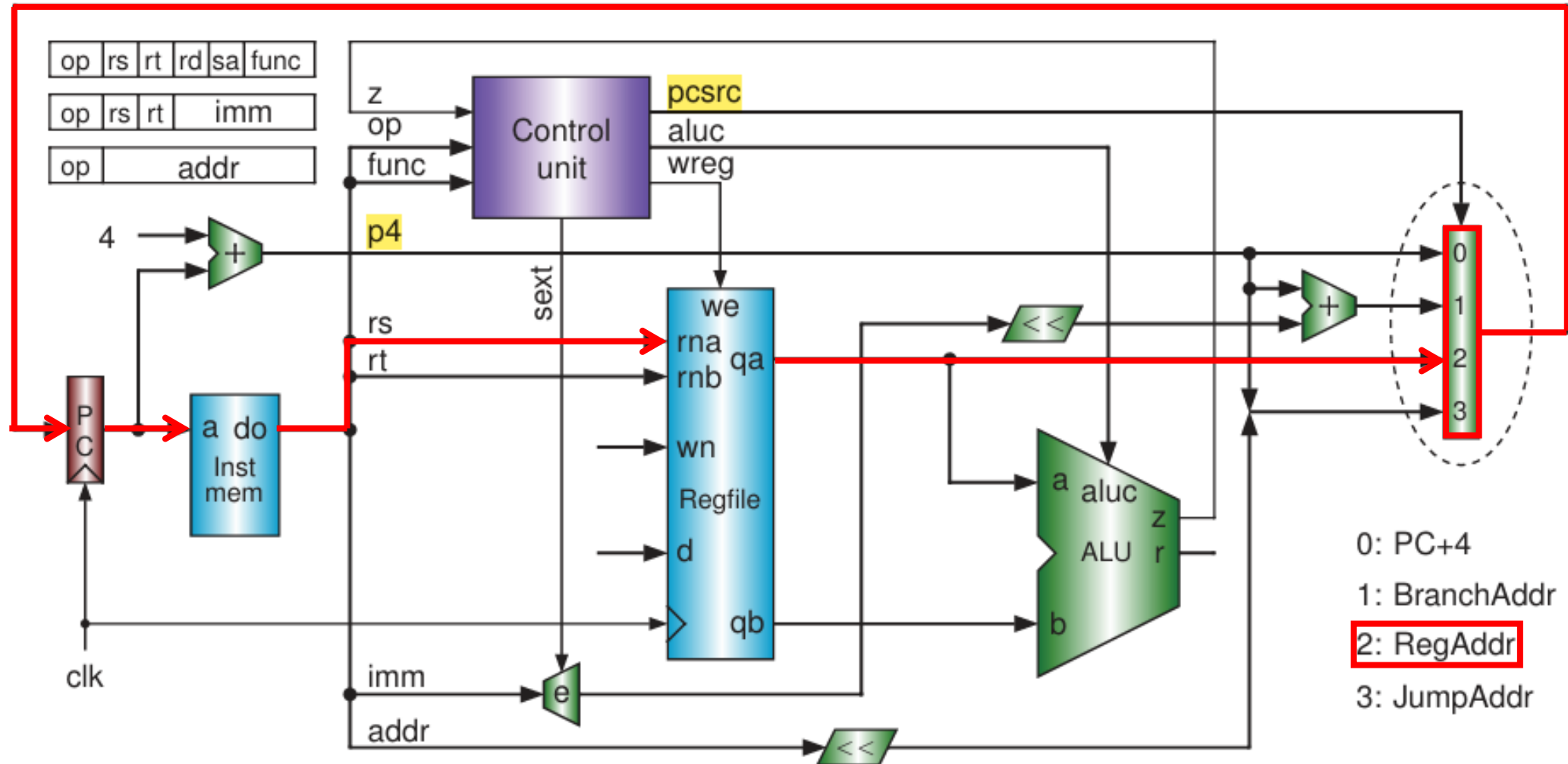


# Next PC

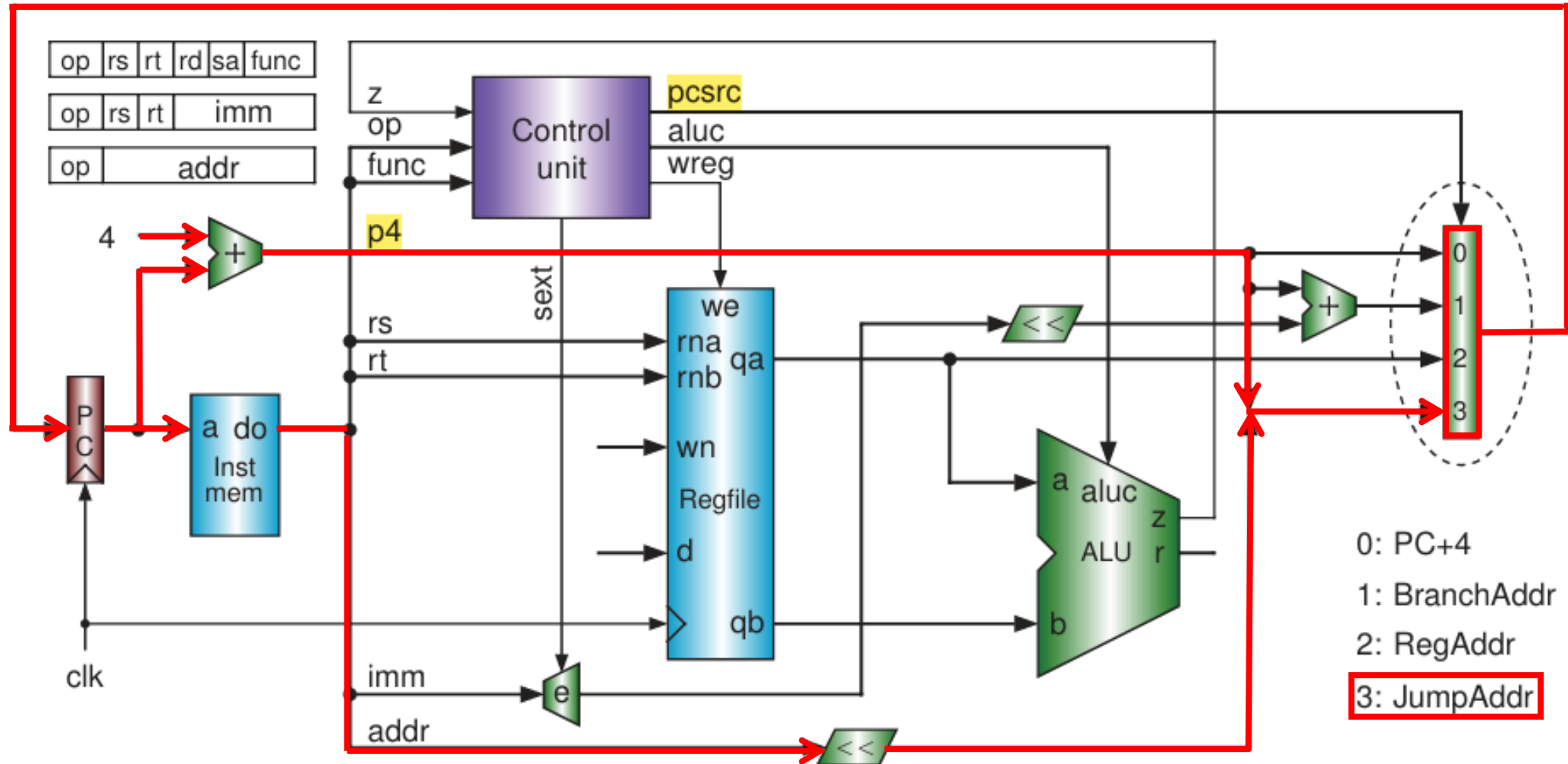
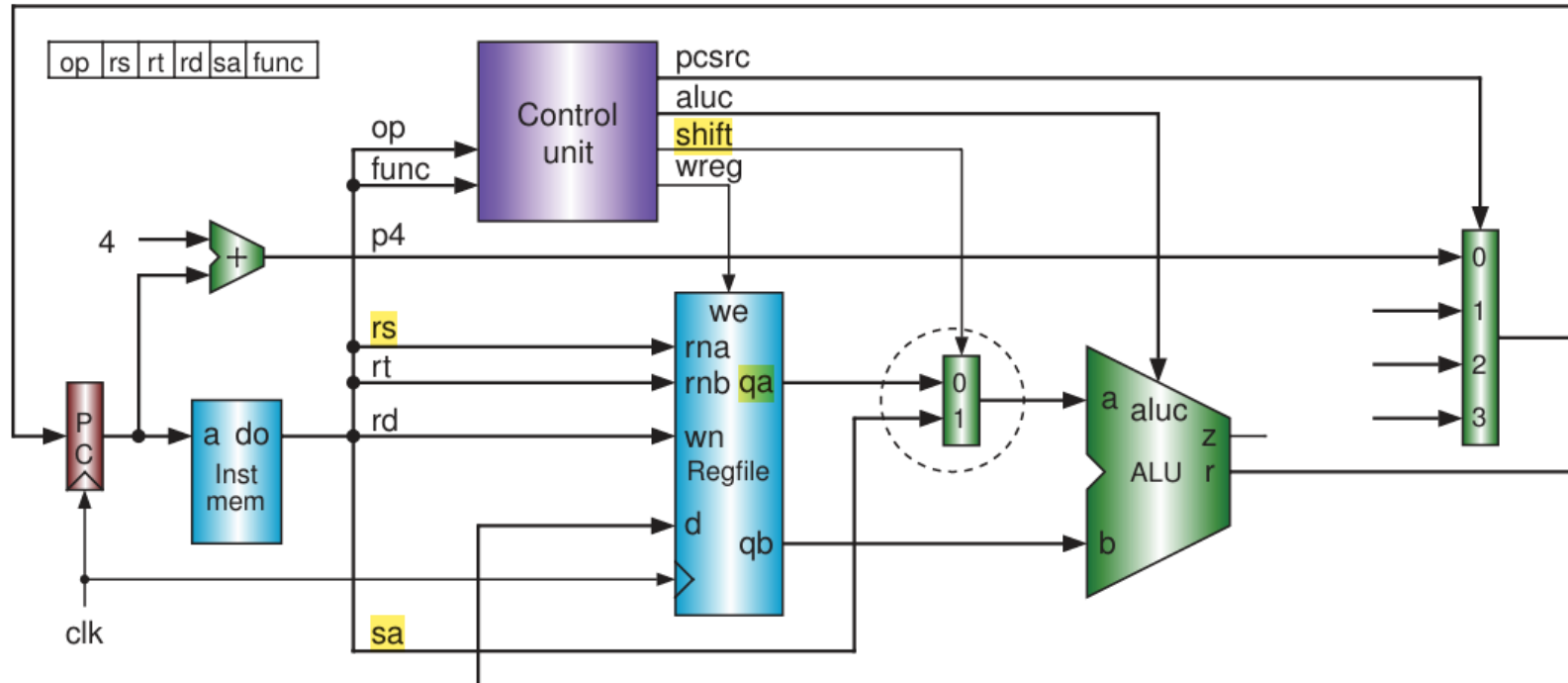
# ALU Input A

- Selection for ALU Input A (Selection signal: *shift*)
- Shift instructions use *sa* as the shift amount.
- Other instructions may use the value in the register *rs*.



`add rd, rs, rt`      `# rd <-- rs + rt`

`sll rd, rt, sa`      `# rd <-- rt << sa`


op	rs	rt	rd	0	func
----	----	----	----	---	------

op	0	rt	rd	sa	func
----	---	----	----	----	------



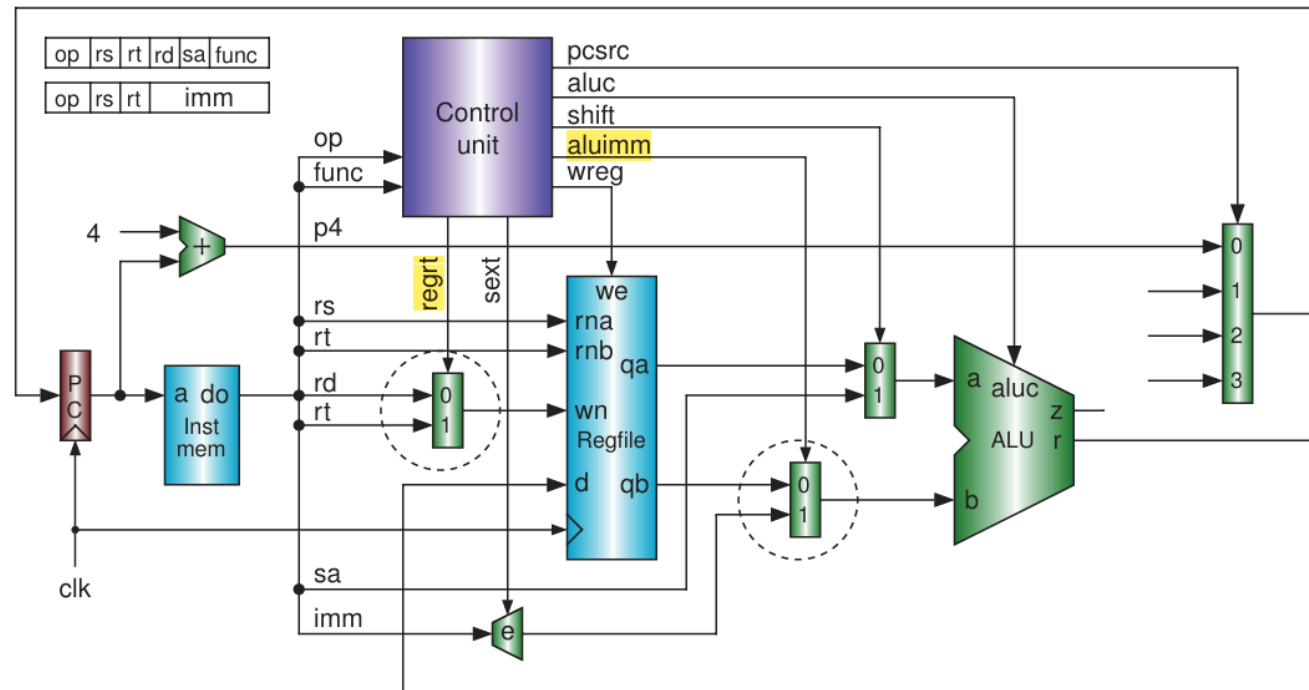
# ALU Input B

- Selection for ALU Input B (Selection Signal: *aluimm* and *regrt*)
- The *immediate* of the I-format instructions will be sent to input b.
- Other instructions may use the value in the register *rt*.


 
```
add rd, rs, rt      # rd <-- rs + rt
addi rt, rs, imm    # rt <-- rs + imm
```




# Register File Inputs

- Selection for Register File Inputs (Selection Signals: *m2reg*, *jal*)
- The data that will be written to the register file may be the output of the ALU, the data in the data memory, or the return address (for *jal*).
- The destination register number may be *rd*, *rt*, or a constant 31.
- The load instruction writes the data read from the memory to the register *rt* of the register file.
- Other instructions may write the output of the ALU to *rd* or *rt*.


`add rd, rs, rt           # rd <-- rs + rt`

`lw rt, imm(rs)          # rt <-- mem[rs+imm]`
 
`jal address # $31 <-- pc + 4; pc <-- address << 2`



# Register File Inputs

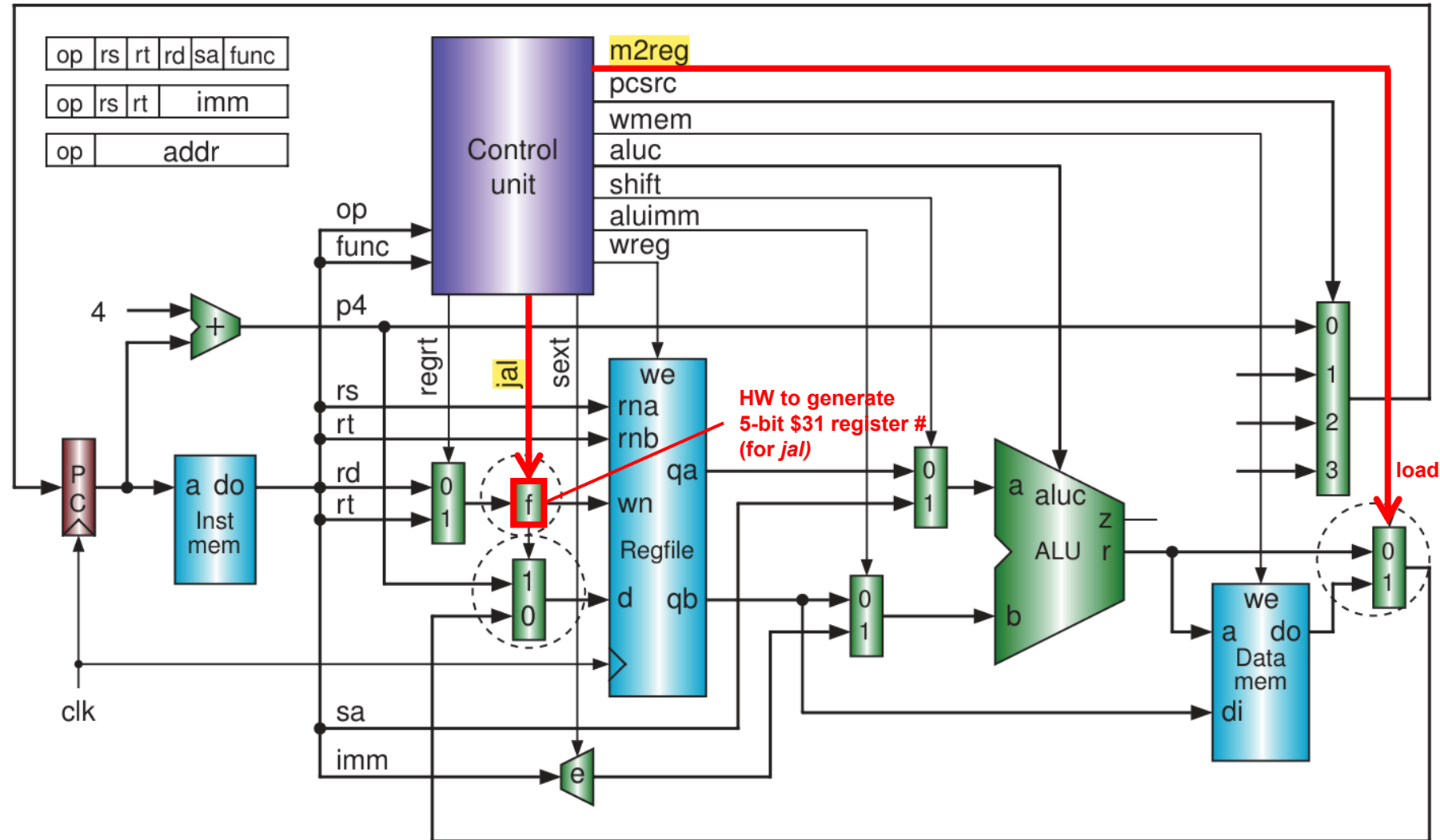

# Control Unit

- Instruction decode

R-format			I- and J-format	
Inst.	op[5:0]	func[5:0]	Inst.	op[5:0]
i_add	000000	100000	i_addi	001000
i_sub	000000	100010	i_andi	001100
i_and	000000	100100	i_ori	001101
i_or	000000	100101	i_xori	001110
i_xor	000000	100110	i_lw	100011
i_sll	000000	000000	i_sw	101011
i_srl	000000	000010	i_beq	000100
i_sra	000000	000011	i_bne	000101
i_jr	000000	001000	i_lui	001111
			i_j	000010
			i_jal	000011

# Control Unit

## ■ Control signals

Signal	Meaning	Action
wreg	Write register	1: write; 0: do not write
regrt	Destination register is <i>rt</i>	1: select <i>rt</i> ; 0: select <i>rd</i>
jal	Subroutine call	1: is <i>jal</i> ; 0: is not <i>jal</i>
m2reg	Save memory data	1: select memory data; 0: select ALU result
shift	ALU A uses <i>sa</i>	1: select <i>sa</i> ; 0: select register data
aluimm	ALU B uses immediate	1: select immediate; 0: select register data
sext	Immediate sign extend	1: sign-extend; 0: zero extend
aluc[3:0]	ALU operation control	x000: ADD;      x100: SUB;      x001: AND x101: OR;      x010: XOR;      x110: LUI 0011: SLL;      0111: SRL;      1111: SRA
wmem	Write memory	1: write memory; 0: do not write
pcsrc[1:0]	Next instruction address	00: select PC+4; 01: branch address 10: register data; 11: jump address

# Control Unit

## ■ Control signals truth table

Inst.	z	wreg	regrt	jal	m2reg	shift	aluimm	sxt	aluc[3:0]	wmem	pcsrc[1:0]
i_add	x	1	0	0	0	0	0	x	x000	0	00
i_sub	x	1	0	0	0	0	0	x	x100	0	00
i_and	x	1	0	0	0	0	0	x	x001	0	00
i_or	x	1	0	0	0	0	0	x	x101	0	00
i_xor	x	1	0	0	0	0	0	x	x010	0	00
i_sll	x	1	0	0	0	1	0	x	0011	0	00
i_srl	x	1	0	0	0	1	0	x	0111	0	00
i_sra	x	1	0	0	0	1	0	x	1111	0	00
i_jr	x	0	x	x	x	x	x	x	x x x x	0	10
i_addi	x	1	1	0	0	0	1	1	x000	0	00
i_andi	x	1	1	0	0	0	1	0	x001	0	00
i_ori	x	1	1	0	0	0	1	0	x101	0	00
i_xori	x	1	1	0	0	0	1	0	x010	0	00
i_lw	x	1	1	0	1	0	1	1	x000	0	00
i_sw	x	0	x	x	x	0	1	1	x000	1	00
i_beq	0	0	x	x	x	0	0	1	x010	0	00
i_beq	1	0	x	x	x	0	0	1	x010	0	01
i_bne	0	0	x	x	x	0	0	1	x010	0	01
i_bne	1	0	x	x	x	0	0	1	x010	0	00
i_lui	x	1	1	0	0	x	1	x	x110	0	00
i_j	x	0	x	x	x	x	x	x	x x x x	0	11
i_jal	x	1	x	1	x	x	x	x	x x x x	0	11

**ALU control signals**  
(wreg, aluc)

**shift control signals**  
(wreg, shift, aluc)

**immediate control signals**  
(wreg, regrt, aluimm, sxt, aluc)

**branch control signals**  
(z, sxt, aluc, pcsrc)

# Control Unit

## Control signals truth table

Inst.	z	wreg	regrt	jal	m2reg	shift	aluimm	sext	aluc[3:0]	wmem	pcsrc[1:0]
i_add	x	1	0	0	0	0	0	x	x000	0	00
i_sub	x	1	0	0	0	0	0	x	x100	0	00
i_and	x	1	0	0	0	0	0	x	x001	0	00
i_or	x	1	0	0	0	0	0	x	x101	0	00
i_xor	x	1	0	0	0	0	0	x	x010	0	00
i_sll	x	1	0	0	0	1	0	x	0011	0	00
i_srl	x	1	0	0	0	1	0	x	0111	0	00
i_sra	x	1	0	0	0	1	0	x	1111	0	00
i_jr	x	0	x	x	x	x	x	x	x x x x	0	10
i_addi	x	1	1	0	0	0	1	1	x000	0	00
i_andi	x	1	1	0	0	0	1	0	x001	0	00
i_ori	x	1	1	0	0	0	1	0	x101	0	00
i_xori	x	1	1	0	0	0	1	0	x010	0	00
i_lw	x	1	1	0	1	0	1	1	x000	0	00
i_sw	x	0	x	x	x	0	1	1	x000	1	00
i_beq	0	0	x	x	x	0	0	1	x010	0	00
i_beq	1	0	x	x	x	0	0	1	x010	0	01
i_bne	0	0	x	x	x	0	0	1	x010	0	01
i_bne	1	0	x	x	x	0	0	1	x010	0	00
i_lui	x	1	1	0	0	x	1	x	x110	0	00
i_j	x	0	x	x	x	x	x	x	x x x x	0	11
i_jal	x	1	x	1	x	x	x	x	x x x x	0	11

jump register (pcsrc)


load (wreg, regrt, m2reg, aluimm, sext)  
store (aluimm, sext, wmem)

load upper immediate (wreg, regrt, aluimm, aluc)

jump (pcsrc)  
jump and link (wreg, jal, pcsrc)

# Single-cycle CPU Design in Verilog HDL

## ■ Dataflow style

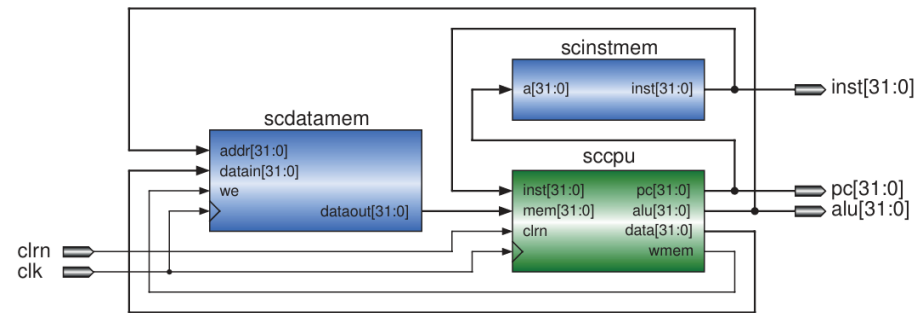

```

1  module sccomp (clk, clrn, inst, pc, aluout, memout);
2      input      clk, clrn;
3      output [31:0] pc;
4      output [31:0] inst;
5      output [31:0] aluout;
6      output [31:0] memout;
7      wire [31:0] data;
8      wire      wmem;
9
10     // cpu
11     sccpu cpu (
12         .clk(clk),
13         .clrn(clrn),
14         .inst(inst),
15         .mem(memout),
16         .pc(pc),
17         .wmem(wmem),
18         .alu(aluout),
19         .data(data)
20     );
21
22     // inst memory
23     scinstmem imem (
24         .a(pc),
25         .inst(inst)
26     );
27
28     // data memory
29     sccdatamem dmem (
30         .clk(clk),
31         .dataout(memout),
32         .datain(data),
33         .addr(aluout),
34         .we(wmem)
35     );
36 endmodule

```

```

1  module sccu_dataflow (op, func, z, wmem, wreg, regrt, m2reg, aluc, shift, aluimm, pcsrc, jal, sext)
2      input [5:0] op, func; // op, func
3      input      z; // alu zero tag
4      output [3:0] aluc; // alu operation control
5      output [1:0] pcsrc; // select pc source
6      output      wreg; // write regfile
7      output      regrt; // dest reg number is rt
8      output      m2reg; // instruction is an lw
9      output      shift; // instruction is a shift
10     output      aluimm; // instruction is an i32
11     output      jal; // instruction is an jal
12     output      sext; // is sign extension
13     output      wmem; // write data memory
14
15     // decode instructions
16     // r format
17     wire rtype = ~lop;
18     wire i_add = rtype & func[5] & ~func[4] & ~func[3] & ~func[2] & ~func[1] & ~func[0];
19     wire i_sub = rtype & func[5] & ~func[4] & ~func[3] & ~func[2] & func[1] & ~func[0];
20     wire i_and = rtype & func[5] & ~func[4] & ~func[3] & func[2] & ~func[1] & ~func[0];
21     wire i_or = rtype & func[5] & ~func[4] & ~func[3] & func[2] & ~func[1] & func[0];
22     wire i_xor = rtype & func[5] & ~func[4] & ~func[3] & func[2] & func[1] & ~func[0];
23     wire i_sll = rtype & ~func[5] & ~func[4] & ~func[3] & ~func[2] & ~func[1] & ~func[0];
24     wire i_srl = rtype & ~func[5] & ~func[4] & ~func[3] & ~func[2] & func[1] & ~func[0];
25     wire i_sra = rtype & ~func[5] & ~func[4] & ~func[3] & ~func[2] & func[1] & func[0];
26     wire i_jr = rtype & ~func[5] & ~func[4] & func[3] & ~func[2] & ~func[1] & ~func[0];
27
28     // i format
29     wire i_addi = ~op[5] & ~op[4] & op[3] & ~op[2] & ~op[1] & ~op[0];
30     wire i_andi = ~op[5] & ~op[4] & op[3] & op[2] & ~op[1] & ~op[0];
31     wire i_ori = ~op[5] & ~op[4] & op[3] & op[2] & op[1] & op[0];
32     wire i_xori = ~op[5] & ~op[4] & op[3] & op[2] & op[1] & ~op[0];
33     wire i_lw = op[5] & ~op[4] & ~op[3] & ~op[2] & op[1] & op[0];
34     wire i_sw = op[5] & ~op[4] & op[3] & ~op[2] & op[1] & op[0];
35     wire i_beq = ~op[5] & ~op[4] & ~op[3] & op[2] & ~op[1] & ~op[0];
36     wire i_bne = ~op[5] & ~op[4] & ~op[3] & op[2] & ~op[1] & op[0];
37     wire i_lui = ~op[5] & ~op[4] & op[3] & op[2] & op[1] & op[0];
38
39     // j format
40     wire i_j = ~op[5] & ~op[4] & ~op[3] & ~op[2] & op[1] & ~op[0];
41     wire i_jal = ~op[5] & ~op[4] & ~op[3] & ~op[2] & op[1] & op[0];
42
43     // generate control signals
44     assign regrt = i_addi | i_andi | i_ori | i_xori | i_lw | i_lui;
45     assign jal = i_jal;
46     assign m2reg = i_lw;
47     assign wmem = i_sw;
48     assign aluc[3] = i_sra;
49     assign aluc[2] = i_sub | i_or | i_srl | i_sra | i_ori | i_lui;
50     assign aluc[1] = i_xor | i_sll | i_srl | i_sra | i_xori | i_beq | i_bne | i_lui;
51     assign aluc[0] = i_and | i_or | i_sll | i_srl | i_sra | i_andi | i_ori;
52     assign shift = i_sll | i_srl | i_sra;
53     assign aluimm = i_addi | i_andi | i_ori | i_xori | i_lw | i_lui | i_sw;
54     assign sext = i_addi | i_lw | i_sw | i_beq | i_bne;
55     assign pcsrc[1] = i_jr | i_j | i_jal;
56     assign pcsrc[0] = i_beq & z | i_bne & ~z | i_j | i_jal;
57     assign wreg = i_add | i_sub | i_and | i_or | i_xor | i_sll |
58         i_srl | i_sra | i_addi | i_andi | i_ori | i_xori |
59         i_lw | i_lui | i_jal;
60 endmodule

```



# Single-cycle CPU Design in Verilog HDL

## ■ Behavioral style

```
1  module sccpu(  
2      input      clk,  
3      input      clrn,  
4      input      [31:0] mem,  
5      input      [31:0] inst,  
6      output reg [31:0] pc,  
7      output reg [31:0] alu,  
8      output      [31:0] data,  
9      output reg      wmem  
10 );  
11  
12     reg      wreg;  
13     reg      [4:0] dest_rn;  
14     reg      [31:0] next_pc;  
15     wire      [31:0] pc4 = pc + 4;
```

```
17     // Instruction Field  
18     wire      [5:0] op   = inst[31:26];  
19     wire      [4:0] rs   = inst[25:21];  
20     wire      [4:0] rt   = inst[20:16];  
21     wire      [4:0] rd   = inst[15:11];  
22     wire      [4:0] sa   = inst[10:06];  
23     wire      [5:0] func = inst[05:00];  
24     wire      [15:0] imm  = inst[15:00];  
25     wire      [25:0] addr = inst[25:00];  
26     wire      sign = inst[15];  
27     wire      [31:0] offset = {{14{sign}},imm,2'b00};  
28     wire      [31:0] j_addr = {pc4[31:28],addr,2'b00};
```

# Single-cycle CPU Design in Verilog HDL

## ■ Behavioral style

```
30 // Instruction Decode
31 // R-format
32 wire i_add = (op == 6'b000000) & (func == 6'b100000);
33 wire i_sub = (op == 6'b000000) & (func == 6'b100010);
34 wire i_and = (op == 6'b000000) & (func == 6'b100100);
35 wire i_or = (op == 6'b000000) & (func == 6'b100101);
36 wire i_xor = (op == 6'b000000) & (func == 6'b100110);
37 wire i_sll = (op == 6'b000000) & (func == 6'b000000);
38 wire i_srl = (op == 6'b000000) & (func == 6'b000010);
39 wire i_sra = (op == 6'b000000) & (func == 6'b000011);
40 wire i_jr = (op == 6'b000000) & (func == 6'b001000);
41 // I-format
42 wire i_addi = (op == 6'b001000);
43 wire i_andi = (op == 6'b001100);
44 wire i_ori = (op == 6'b001101);
45 wire i_xori = (op == 6'b001110);
46 wire i_lw = (op == 6'b100011);
47 wire i_sw = (op == 6'b101011);
48 wire i_beq = (op == 6'b000100);
49 wire i_bne = (op == 6'b000101);
50 wire i_lui = (op == 6'b001111);
51 // J-format
52 wire i_j = (op == 6'b000010);
53 wire i_jal = (op == 6'b000011);
```

```
55 // Program Counter
56 always @(posedge clk or negedge clrn) begin
57     if (!clrn) begin
58         pc <= 0;
59     end else begin
60         pc <= next_pc;
61     end
62 end
63
64 // Data written into Register File
65 wire [31:0] data_to_regfile = i_lw ? mem : alu;
66
67 // Register File
68 reg [31:0] regfile [1:31];
69 wire [31:0] a = (rs == 0) ? 0 : regfile[rs];
70 wire [31:0] b = (rt == 0) ? 0 : regfile[rt];
71
72 integer i; // to initialize regfile or the error occurs
73 always @(posedge clk or negedge clrn) begin
74     if (!clrn) begin
75         for (i = 1; i < 32; i = i + 1) begin
76             regfile[i] <= 0;
77         end
78     end else if (wreg && (dest_rn != 0)) begin
79         regfile[dest_rn] <= data_to_regfile;
80     end
81 end
82
83 // Output signals
84 assign data = b;
```

# Single-cycle CPU Design in Verilog HDL

## ■ Behavioral style

```
87 always @(*) begin
88     alu = 0;
89     dest_rn = rd;
90     wreg = 0;
91     wmem = 0;
92     next_pc = pc4;
93
94     case (1'b1)
95     i_add: begin
96         alu = a + b;
97         wreg = 1;
98     end
99
100    i_sub: begin
101        alu = a - b;
102        wreg = 1;
103    end
104
105    i_and: begin
106        alu = a & b;
107        wreg = 1;
108    end
109
110    i_or: begin
111        alu = a | b;
112        wreg = 1;
113    end
114
115    i_xor: begin
116        alu = a ^ b;
117        wreg = 1;
118    end
119
120    i_sll: begin
121        alu = b << sa;
122        wreg = 1;
123    end
```

```
125
126
127 i_srl: begin
128     alu = b >> sa;
129     wreg = 1;
130 end
131
132 i_sra: begin
133     alu = $signed(b) >>> sa;
134     wreg = 1;
135 end
136
137 i_jr: begin
138     next_pc = a;
139 end
140
141 i_addi: begin
142     alu = a + {{16{sign}}},imm;
143     dest_rn = rt;
144     wreg = 1;
145 end
146
147 i_andi: begin
148     alu = a & {16'h0,imm};
149     dest_rn = rt;
150     wreg = 1;
151 end
152
153 i_ori: begin
154     alu = a | {16'h0,imm};
155     dest_rn = rt;
156     wreg = 1;
157 end
158
159 i_xori: begin
160     alu = a ^ {16'h0,imm};
161     dest_rn = rt;
162     wreg = 1;
163 end
```

```
163
164 i_lw: begin
165     alu = a + {{16{sign}}},imm;
166     dest_rn = rt;
167     wreg = 1;
168 end
169
170 i_sw: begin
171     alu = a + {{16{sign}}},imm;
172     dest_rn = rt;
173     wmem = 1;
174     wreg = 1;
175 end
176
177 i_beq: begin
178     if (a == b) begin
179         next_pc = pc4 + offset;
180     end
181 end
182
183 i_bne: begin
184     if (a != b) begin
185         next_pc = pc4 + offset;
186     end
187 end
188
189 i_lui: begin
190     alu = {imm,16'h0};
191     wreg = 1;
192 end
193
194 i_j: begin
195     next_pc = j_addr;
196 end
197
198 i_jal: begin
199     alu = pc4;
200     wreg = 1;
201     dest_rn = 5'd31;
202     next_pc = j_addr;
203 end
```





# Simulation

## ■ Test program

(pc) label instruction

```

    
(00) main:    lui    $1, 0
(04)         ori    $4, $1, 80
(08)         addi   $5, $0, 4
(0c) call:    jal    sum
(10)         sw     $2, 0($4)
(14)         lw     $9, 0($4)
(18)         sub    $8, $9, $4
(1c)         addi   $5, $0, 3
(20) loop2:   addi   $5, $5, -1
(24)         ori    $8, $5, 0xffff
(28)         xori   $8, $8, 0x5555
(2c)         addi   $9, $0, -1
(30)         andi   $10, $9, 0xffff
(34)         or     $6, $10, $9
(38)         xor    $8, $10, $9
(3c)         and    $7, $10, $6
    
```



# Simulation

## ■ Test program

(pc)	label	instruction	
(00)	main:	lui \$1, 0	
(04)		ori \$4, \$1, 80	
(08)		addi \$5, \$0, 4	
(0c)	call:	jal sum	(40)
(10)		sw \$2, 0(\$4)	(44)
(14)		lw \$9, 0(\$4)	(48)
(18)		sub \$8, \$9, \$4	(4c)
(1c)		addi \$5, \$0, 3	(50)
(20)	loop2:	addi \$5, \$5, -1	(54)
(24)		ori \$8, \$5, 0xff	(58)
(28)		xori \$8, \$8, 0x55	(5c)
(2c)		addi \$9, \$0, -1	(60)
(30)		andi \$10, \$9, 0xff	(64)
(34)		or \$6, \$10, \$9	(68)
(38)		xor \$8, \$10, \$9	(6c)
(3c)		and \$7, \$10, \$6	(70)
			(74)
			(78)
			(7c)
			(80)
			(84)
			(88)
			(8c)
			(90)
			(94)
			(98)
			(9c)
			(a0)
			(a4)
			(a8)
			(ac)
			(b0)
			(b4)
			(b8)
			(bc)
			(c0)
			(c4)
			(c8)
			(cc)
			(d0)
			(d4)
			(d8)
			(dc)
			(e0)
			(e4)
			(e8)
			(ec)
			(f0)
			(f4)
			(f8)
			(fc)

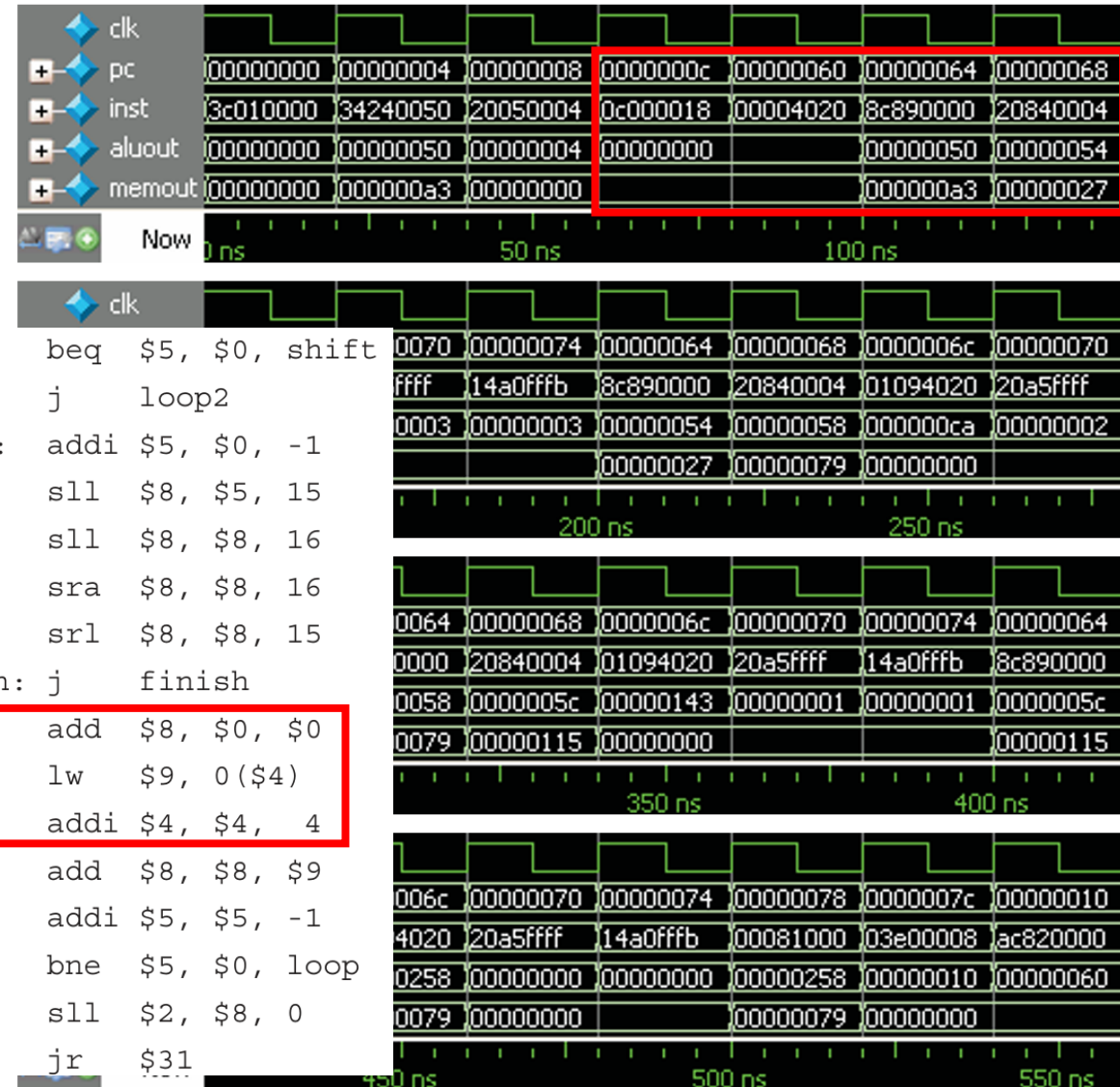







# Simulation

## ■ Test program

```

  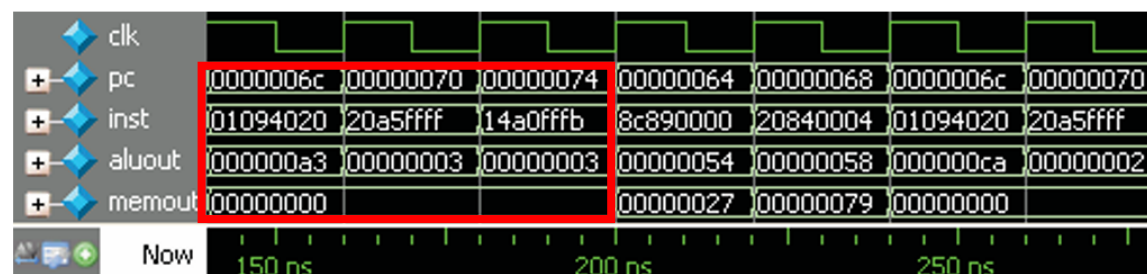 (40)          beq  $5, $0, shift
(44)          j    loop2
(48) shift:    addi $5, $0, -1
(4c)          sll  $8, $5, 15
(50)          sll  $8, $8, 16
(54)          sra  $8, $8, 16
(58)          srl  $8, $8, 15
(5c) finish:  j    finish
(60) sum:      add  $8, $0, $0
(64) loop:     lw   $9, 0($4)
(68)          addi $4, $4, 4
(6c)          add  $8, $8, $9
(70)          addi $5, $5, -1
(74)          bne  $5, $0, loop
(78)          sll  $2, $8, 0
(7c)          jr   $31
    
```







# Simulation

## ■ Test program

```

    (40)          beq  $5, $0, shift
(44)          j    loop2
(48) shift:    addi $5, $0, -1
(4c)          sll  $8, $5, 15
(50)          sll  $8, $8, 16
(54)          sra  $8, $8, 16
(58)          srl  $8, $8, 15
(5c) finish:  j    finish
(60) sum:      add  $8, $0, $0
(64) loop:     lw   $9, 0($4)
(68)          addi $4, $4, 4
(6c)          add  $8, $8, $9
(70)          addi $5, $5, -1
(74)          bne  $5, $0, loop
(78)          sll  $2, $8, 0
(7c)          jr   $31
    
```







# Simulation

## ■ Test program

```

  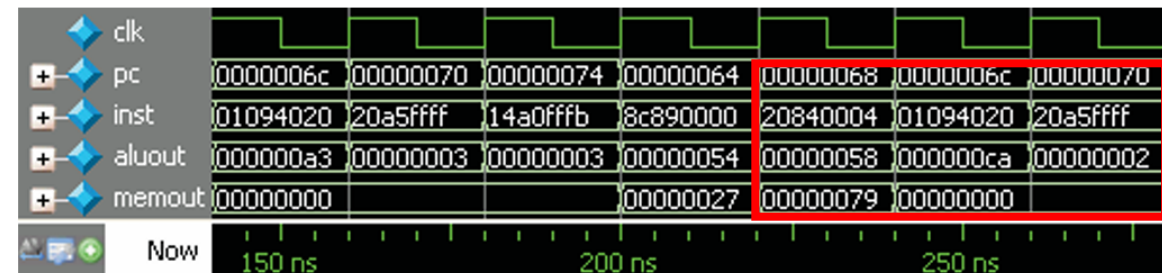 (40)          beq  $5, $0, shift
(44)          j    loop2
(48) shift:    addi $5, $0, -1
(4c)          sll  $8, $5, 15
(50)          sll  $8, $8, 16
(54)          sra  $8, $8, 16
(58)          srl  $8, $8, 15
(5c) finish:  j    finish
(60) sum:      add  $8, $0, $0
(64) loop:     lw   $9, 0($4)
(68)          addi $4, $4, 4
(6c)          add  $8, $8, $9
(70)          addi $5, $5, -1
(74)          bne  $5, $0, loop
(78)          sll  $2, $8, 0
(7c)          jr   $31
    
```









# Simulation

## ■ Test program

```

    (40)          beq  $5, $0, shift
(44)          j    loop2
(48) shift:    addi $5, $0, -1
(4c)          sll  $8, $5, 15
(50)          sll  $8, $8, 16
(54)          sra  $8, $8, 16
(58)          srl  $8, $8, 15
(5c) finish:  j    finish
(60) sum:      add  $8, $0, $0
(64) loop:     lw   $9, 0($4)
(68)          addi $4, $4, 4
(6c)          add  $8, $8, $9
(70)          addi $5, $5, -1
(74)          bne  $5, $0, loop
(78)          sll  $2, $8, 0
(7c)          jr   $31
    
```







# Simulation

## ■ Test program

```

 
 
 
 
(40)          beq  $5, $0, shift
(44)          j    loop2
(48) shift:    addi $5, $0, -1
(4c)          sll  $8, $5, 15
(50)          sll  $8, $8, 16
(54)          sra  $8, $8, 16
(58)          srl  $8, $8, 15
(5c) finish:  j    finish
(60) sum:      add  $8, $0, $0
(64) loop:     lw   $9, 0($4)
(68)          addi $4, $4, 4
(6c)          add  $8, $8, $9
(70)          addi $5, $5, -1
(74)          bne  $5, $0, loop
(78)          sll  $2, $8, 0
(7c)          jr   $31
    
```



# Simulation
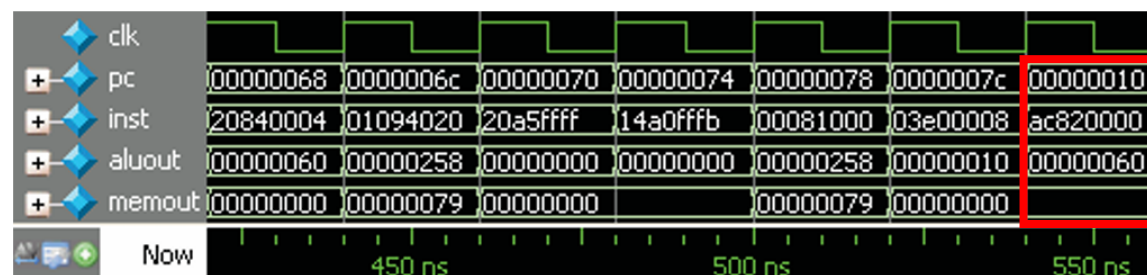   
## ■ Test program


```
(pc) label    instruction
(00) main:    lui    $1, 0
(04)          ori    $4, $1, 80
(08)          addi   $5, $0, 4
(0c) call:    jal    sum
(10)          sw     $2, 0($4)
(14)          lw     $9, 0($4)
(18)          sub    $8, $9, $4
(1c)          addi   $5, $0, 3
(20) loop2:   addi   $5, $5, -1
(24)          ori    $8, $5, 0xffff
(28)          xori   $8, $8, 0x5555
(2c)          addi   $9, $0, -1
(30)          andi   $10, $9, 0xffff
(34)          or     $6, $10, $9
(38)          xor    $8, $10, $9
(3c)          and    $7, $10, $6
```



# Simulation

## ■ Test program

(pc) label	instruction	(40)	beq \$5, \$0, shift
(00) main:	lui \$1, 0	(44)	j loop2
(04)	ori \$4, \$1, 80	(48) shift:	addi \$5, \$0, -1
(08)	addi \$5, \$0, 4	(4c)	sll \$8, \$5, 15
(0c) call:	jal sum	(50)	sll \$8, \$8, 16
(10)	sw \$2, 0(\$4)	(54)	sra \$8, \$8, 16
(14)	lw \$9, 0(\$4)	(58)	srl \$8, \$8, 15
(18)	sub \$8, \$9, \$4	(5c) finish:	j finish
(1c)	addi \$5, \$0, 3	(60) sum:	add \$8, \$0, \$0
(20) loop2:	addi \$5, \$5, -1	(64) loop:	lw \$9, 0(\$4)
(24)	ori \$8, \$5, 0xffff	(68)	addi \$4, \$4, 4
(28)	xori \$8, \$8, 0x5555	(6c)	add \$8, \$8, \$9
(2c)	addi \$9, \$0, -1	(70)	addi \$5, \$5, -1
(30)	andi \$10, \$9, 0xffff	(74)	bne \$5, \$0, loop
(34)	or \$6, \$10, \$9	(78)	sll \$2, \$8, 0
(38)	xor \$8, \$10, \$9	(7c)	jr \$31
(3c)	and \$7, \$10, \$6		

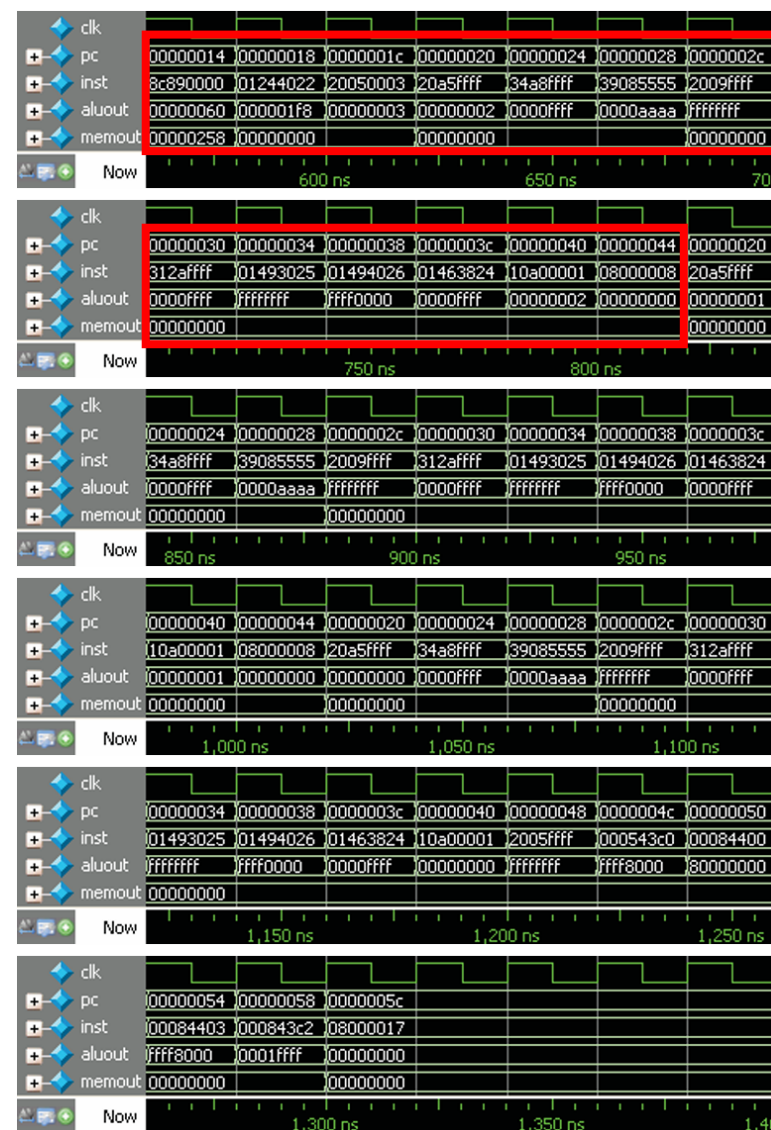



# Simulation

## ■ Test program

(pc) label	instruction	(40)	beq \$5, \$0, shift
(00) main:	lui \$1, 0	(44)	j <b>loop2</b>
(04)	ori \$4, \$1, 80	(48) shift:	addi \$5, \$0, -1
(08)	addi \$5, \$0, 4	(4c)	sll \$8, \$5, 15
(0c) call:	jal sum	(50)	sll \$8, \$8, 16
(10)	sw \$2, 0(\$4)	(54)	sra \$8, \$8, 16
(14)	lw \$9, 0(\$4)	(58)	srl \$8, \$8, 15
(18)	sub \$8, \$9, \$4	(5c) finish:	j finish
(1c)	addi \$5, \$0, 3	(60) sum:	add \$8, \$0, \$0
<b>(20) loop2:</b>	<b>addi \$5, \$5, -1</b>	(64) loop:	lw \$9, 0(\$4)
(24)	ori \$8, \$5, 0xffff	(68)	addi \$4, \$4, 4
(28)	xori \$8, \$8, 0x5555	(6c)	add \$8, \$8, \$9
(2c)	addi \$9, \$0, -1	(70)	addi \$5, \$5, -1
(30)	andi \$10, \$9, 0xffff	(74)	bne \$5, \$0, loop
(34)	or \$6, \$10, \$9	(78)	sll \$2, \$8, 0
(38)	xor \$8, \$10, \$9	(7c)	jr \$31
(3c)	and \$7, \$10, \$6		



# Simulation

## ■ Test program

(pc) label	instruction	(40)	beq \$5, \$0, shift
(00) main:	lui \$1, 0	(44)	j loop2
(04)	ori \$4, \$1, 80	(48) shift:	addi \$5, \$0, -1
(08)	addi \$5, \$0, 4	(4c)	sll \$8, \$5, 15
(0c) call:	jal sum	(50)	sll \$8, \$8, 16
(10)	sw \$2, 0(\$4)	(54)	sra \$8, \$8, 16
(14)	lw \$9, 0(\$4)	(58)	srl \$8, \$8, 15
(18)	sub \$8, \$9, \$4	(5c) finish:	j finish
(1c)	addi \$5, \$0, 3	(60) sum:	add \$8, \$0, \$0
(20) loop2:	addi \$5, \$5, -1	(64) loop:	lw \$9, 0(\$4)
(24)	ori \$8, \$5, 0xffff	(68)	addi \$4, \$4, 4
(28)	xori \$8, \$8, 0x5555	(6c)	add \$8, \$8, \$9
(2c)	addi \$9, \$0, -1	(70)	addi \$5, \$5, -1
(30)	andi \$10, \$9, 0xffff	(74)	bne \$5, \$0, loop
(34)	or \$6, \$10, \$9	(78)	sll \$2, \$8, 0
(38)	xor \$8, \$10, \$9	(7c)	jr \$31
(3c)	and \$7, \$10, \$6		



# Simulation

## ■ Test program


(pc) label	instruction	(40)	beq \$5, \$0, shift
(00) main:	lui \$1, 0	(44)	j <b>loop2</b>
(04)	ori \$4, \$1, 80	(48) shift:	addi \$5, \$0, -1
(08)	addi \$5, \$0, 4	(4c)	sll \$8, \$5, 15
(0c) call:	jal sum	(50)	sll \$8, \$8, 16
(10)	sw \$2, 0(\$4)	(54)	sra \$8, \$8, 16
(14)	lw \$9, 0(\$4)	(58)	srl \$8, \$8, 15
(18)	sub \$8, \$9, \$4	(5c) finish:	j finish
(1c)	addi \$5, \$0, 3	(60) sum:	add \$8, \$0, \$0
<b>(20) loop2:</b>	<b>addi \$5, \$5, -1</b>	(64) loop:	lw \$9, 0(\$4)
(24)	ori \$8, \$5, 0xffff	(68)	addi \$4, \$4, 4
(28)	xori \$8, \$8, 0x5555	(6c)	add \$8, \$8, \$9
(2c)	addi \$9, \$0, -1	(70)	addi \$5, \$5, -1
(30)	andi \$10, \$9, 0xffff	(74)	bne \$5, \$0, loop
(34)	or \$6, \$10, \$9	(78)	sll \$2, \$8, 0
(38)	xor \$8, \$10, \$9	(7c)	jr \$31
(3c)	and \$7, \$10, \$6		



# Simulation

## ■ Test program

(pc)	label	instruction	(40)	beq \$5, \$0, shift
(00)	main:	lui \$1, 0	(44)	j loop2
(04)		ori \$4, \$1, 80	(48)	shift: addi \$5, \$0, -1
(08)		addi \$5, \$0, 4	(4c)	sll \$8, \$5, 15
(0c)	call:	jal sum	(50)	sll \$8, \$8, 16
(10)		sw \$2, 0(\$4)	(54)	sra \$8, \$8, 16
(14)		lw \$9, 0(\$4)	(58)	srl \$8, \$8, 15
(18)		sub \$8, \$9, \$4	(5c)	finish: j finish
(1c)		addi \$5, \$0, 3	(60)	sum: add \$8, \$0, \$0
(20)	loop2:	addi \$5, \$5, -1	(64)	loop: lw \$9, 0(\$4)
(24)		ori \$8, \$5, 0xffff	(68)	addi \$4, \$4, 4
(28)		xori \$8, \$8, 0x5555	(6c)	add \$8, \$8, \$9
(2c)		addi \$9, \$0, -1	(70)	addi \$5, \$5, -1
(30)		andi \$10, \$9, 0xffff	(74)	bne \$5, \$0, loop
(34)		or \$6, \$10, \$9	(78)	sll \$2, \$8, 0
(38)		xor \$8, \$10, \$9	(7c)	jr \$31
(3c)		and \$7, \$10, \$6		

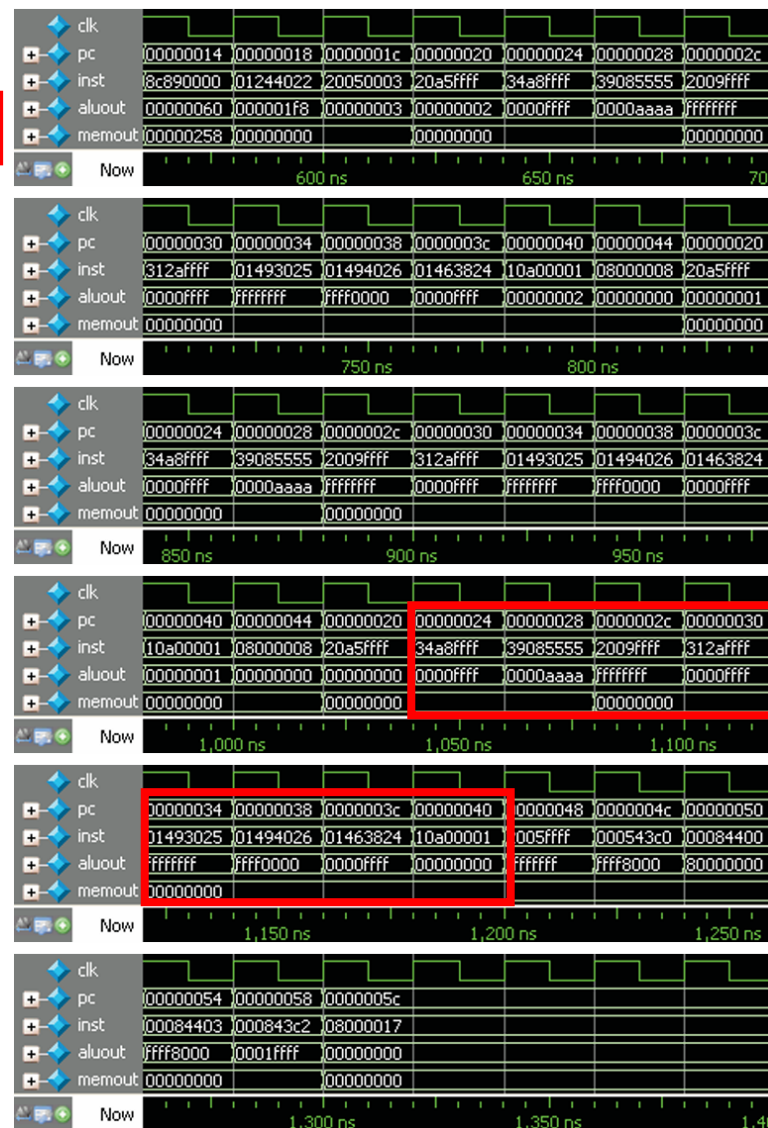



# Simulation

## ■ Test program

(pc) label	instruction	(40)	beq \$5, \$0, <b>shift</b>
(00) main:	lui \$1, 0	(44)	j loop2
(04)	ori \$4, \$1, 80	<b>(48) shift:</b>	<b>addi \$5, \$0, -1</b>
(08)	addi \$5, \$0, 4	(4c)	sll \$8, \$5, 15
(0c) call:	jal sum	(50)	sll \$8, \$8, 16
(10)	sw \$2, 0(\$4)	(54)	sra \$8, \$8, 16
(14)	lw \$9, 0(\$4)	(58)	srl \$8, \$8, 15
(18)	sub \$8, \$9, \$4	(5c) finish:	j finish
(1c)	addi \$5, \$0, 3	(60) sum:	add \$8, \$0, \$0
(20) loop2:	addi \$5, \$5, -1	(64) loop:	lw \$9, 0(\$4)
(24)	ori \$8, \$5, 0xffff	(68)	addi \$4, \$4, 4
(28)	xori \$8, \$8, 0x5555	(6c)	add \$8, \$8, \$9
(2c)	addi \$9, \$0, -1	(70)	addi \$5, \$5, -1
(30)	andi \$10, \$9, 0xffff	(74)	bne \$5, \$0, loop
(34)	or \$6, \$10, \$9	(78)	sll \$2, \$8, 0
(38)	xor \$8, \$10, \$9	(7c)	jr \$31
(3c)	and \$7, \$10, \$6		



# Simulation


## ■ Test program

(pc) label	instruction	(40)	beq \$5, \$0, shift
(00) main:	lui \$1, 0	(44)	j loop2
(04)	ori \$4, \$1, 80	(48) shift:	addi \$5, \$0, -1
(08)	addi \$5, \$0, 4	(4c)	sll \$8, \$5, 15
(0c) call:	jal sum	(50)	sll \$8, \$8, 16
(10)	sw \$2, 0(\$4)	(54)	sra \$8, \$8, 16
(14)	lw \$9, 0(\$4)	(58)	srl \$8, \$8, 15
(18)	sub \$8, \$9, \$4	(5c) finish:	j finish
(1c)	addi \$5, \$0, 3	(60) sum:	add \$8, \$0, \$0
(20) loop2:	addi \$5, \$5, -1	(64) loop:	lw \$9, 0(\$4)
(24)	ori \$8, \$5, 0xffff	(68)	addi \$4, \$4, 4
(28)	xori \$8, \$8, 0x5555	(6c)	add \$8, \$8, \$9
(2c)	addi \$9, \$0, -1	(70)	addi \$5, \$5, -1
(30)	andi \$10, \$9, 0xffff	(74)	bne \$5, \$0, loop
(34)	or \$6, \$10, \$9	(78)	sll \$2, \$8, 0
(38)	xor \$8, \$10, \$9	(7c)	jr \$31
(3c)	and \$7, \$10, \$6		


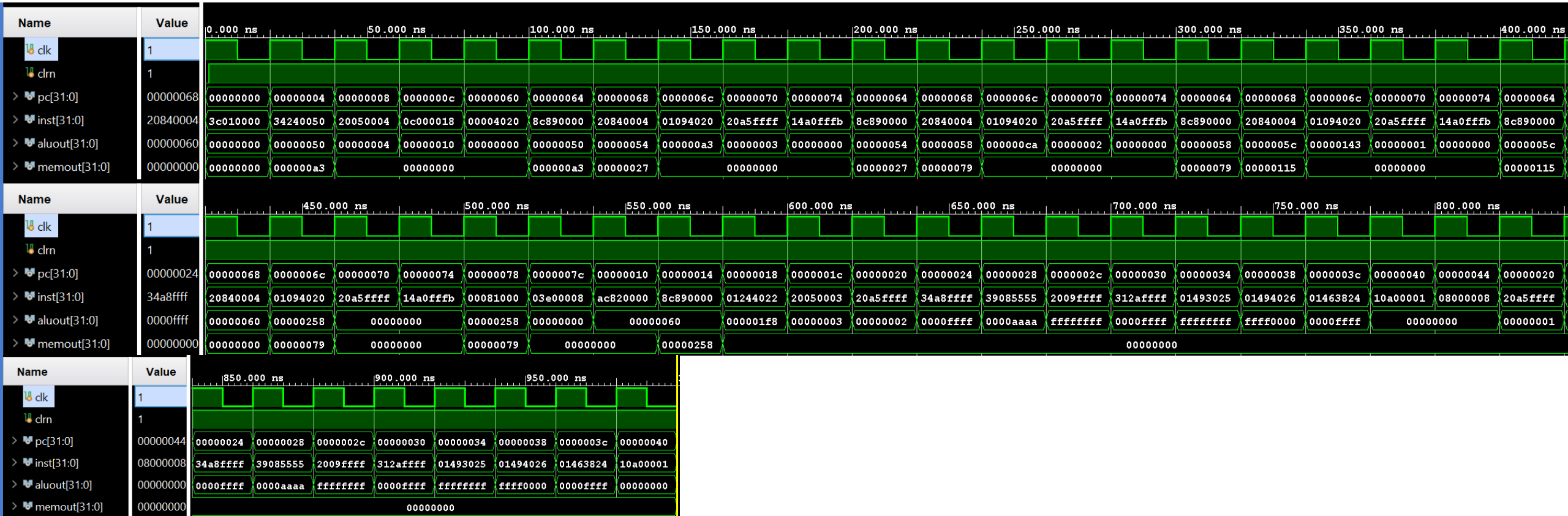
# Simulation

- Simulation results of the behavioral design.



# References

---

[1] Yamin Li, *Computer Principles and Design in Verilog HDL*, Wiley, 2016.